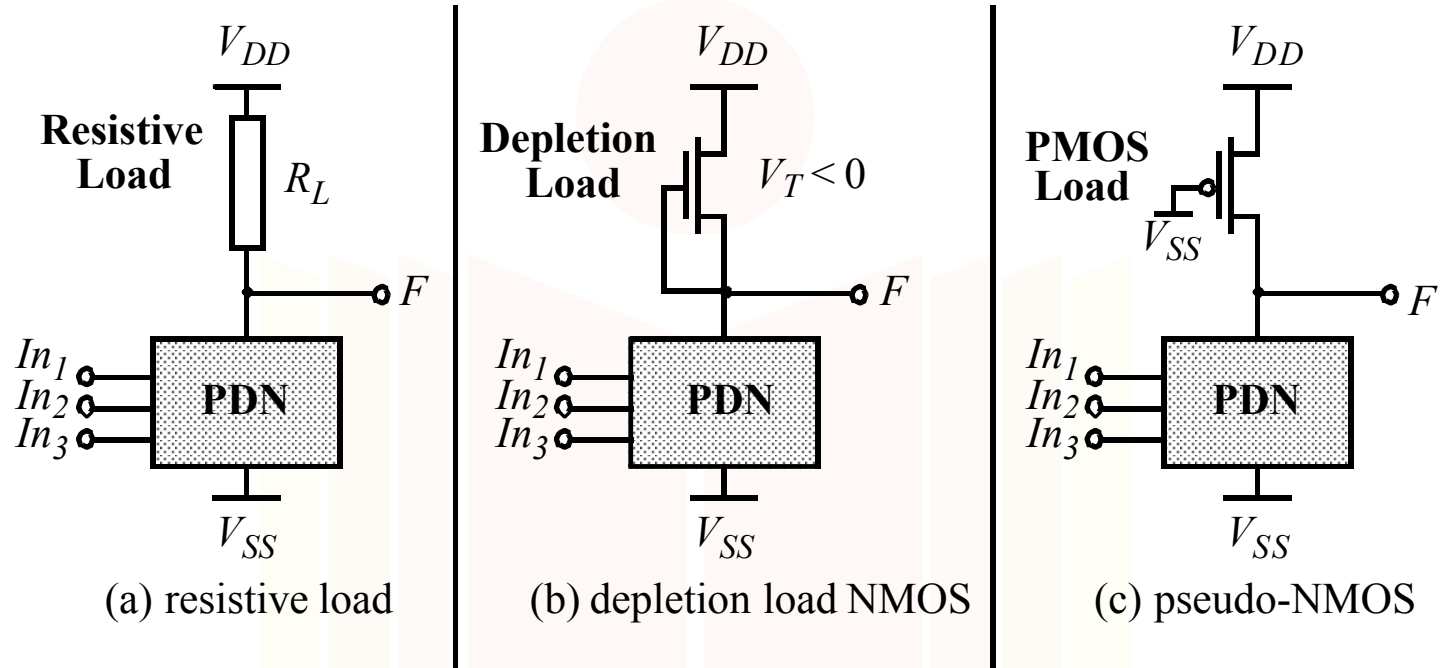


Introduction to VLSI Design

Lecture 19



Material primarily from textbook and lecture slides for Rabaey et. al.
Digital Integrated Circuits, 2nd Edition (2002) and other online resources

Ratioed Logic







Goal: to reduce the number of devices over complementary CMOS


Pass Transistor Logic

  


Complementary Pass Transistor Logic

    

AND/NAND

 


OR/NOR

 


XOR/NXOR

Cascading Pass Transistors

 

Dynamic CMOS

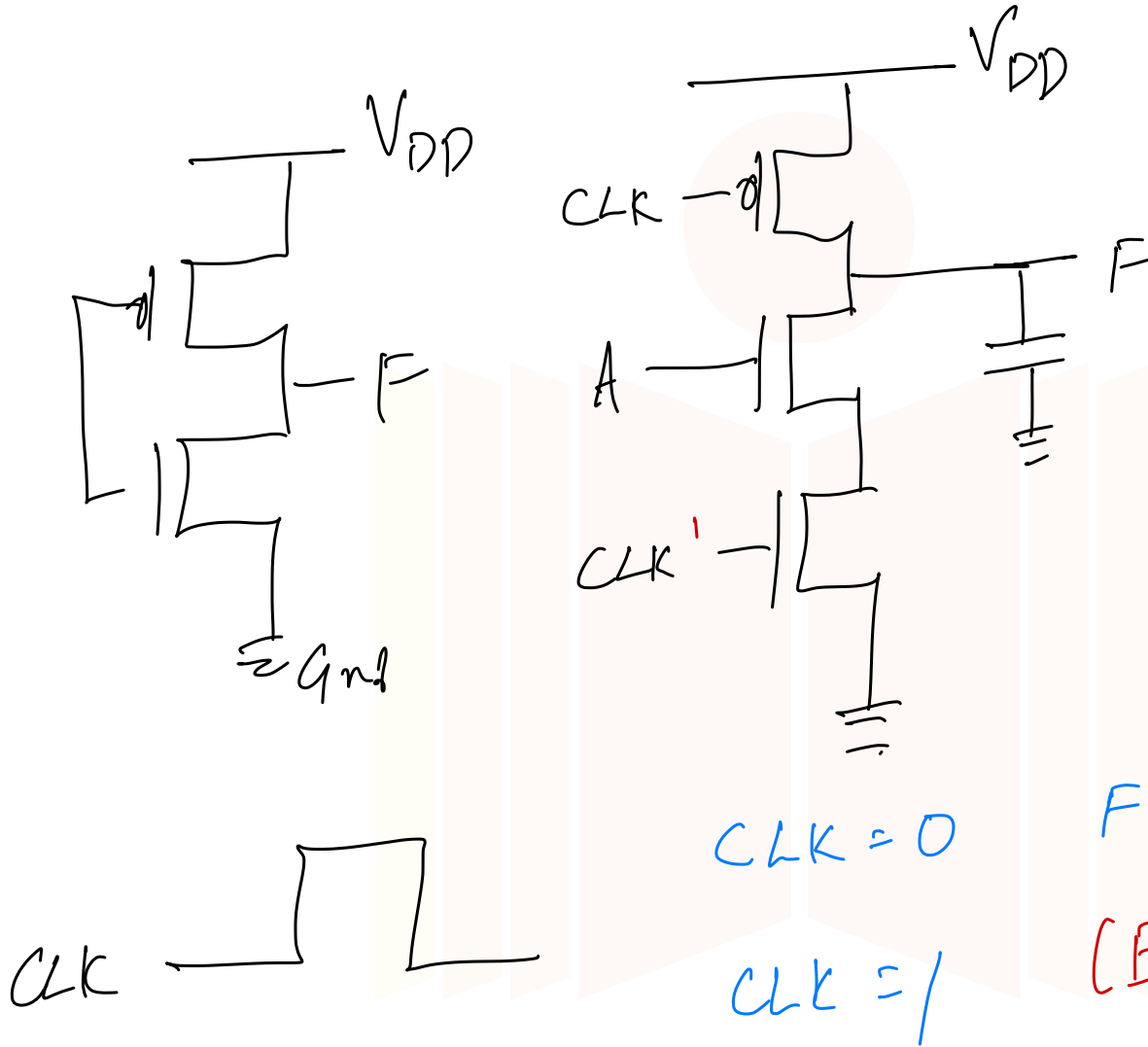


A	CLK	F
X	0	1
X	0	1
0	1	1
1	1	0


$F = 1$ (Pre charge)

(Evaluate)

Dynamic CMOS

 


Dynamic CMOS

 

Dynamic CMOS

 - In **static** circuits at every point in time (except when switching) the output is connected to either GND or V_{DD} via a low resistance path.
 - fan-in of n requires $2n$ (n N-type + n P-type) devices
- **Dynamic** circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.
 - requires on $n + 2$ ($n+1$ N-type + 1 P-type) transistors




Two phase operation

Precharge ($CLK = 0$)

Evaluate ($CLK = 1$)


Dynamic Gate - Example

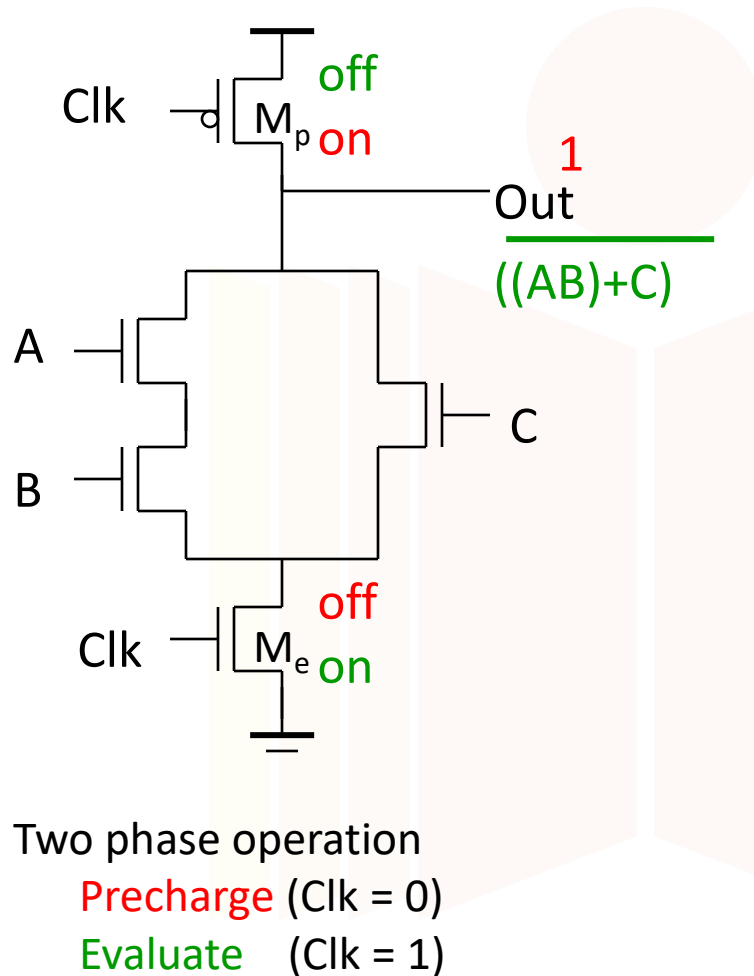

- Once the output of a dynamic gate is discharged, it cannot be charged again until the next precharge operation.
- Inputs to the gate can make at most one transition during evaluation.
- Output can be in the high impedance state during and after evaluation (PDN off), state is stored on CL




Properties of Dynamic Gates

- Logic function is implemented by PDN only
 - $N+2$ transistors Vs $2N$ transistors for CMOS
- Full swing outputs ($V_{OL}=GND$ and $V_{OH}=V_{DD}$)
- Faster switching speeds (reduced C_{in} and C_{out})
- Overall power dissipation usually higher than CMOS
- PDN starts to work as soon as the input signals exceed V_{Tn} , so V_M , V_{IH} and V_{IL} equal to V_{Tn}
- Needs a precharge/evaluate clock

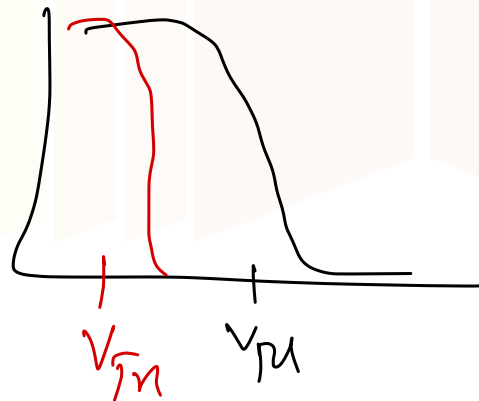


Issues with Dynamic Logic

   - Charge leakage due to sub-threshold conduction
 - Operate circuits at the highest possible frequency
 - Level restoring circuits
- Charge sharing between C_L and internal node capacitances
- Clock feedthrough




Cascading Dynamic Gates

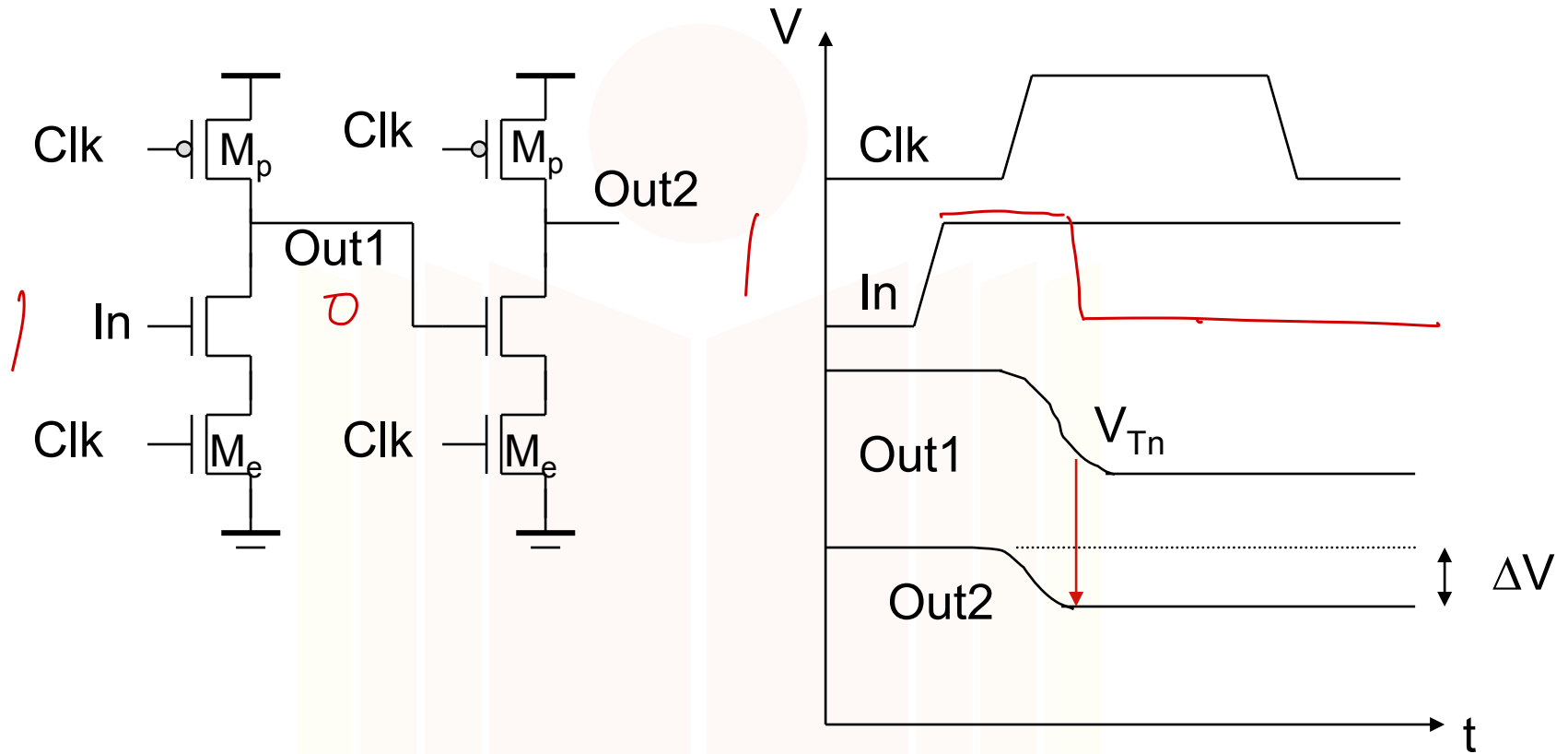


Only 0 \rightarrow 1 transitions allowed at inputs!

Domino Logic

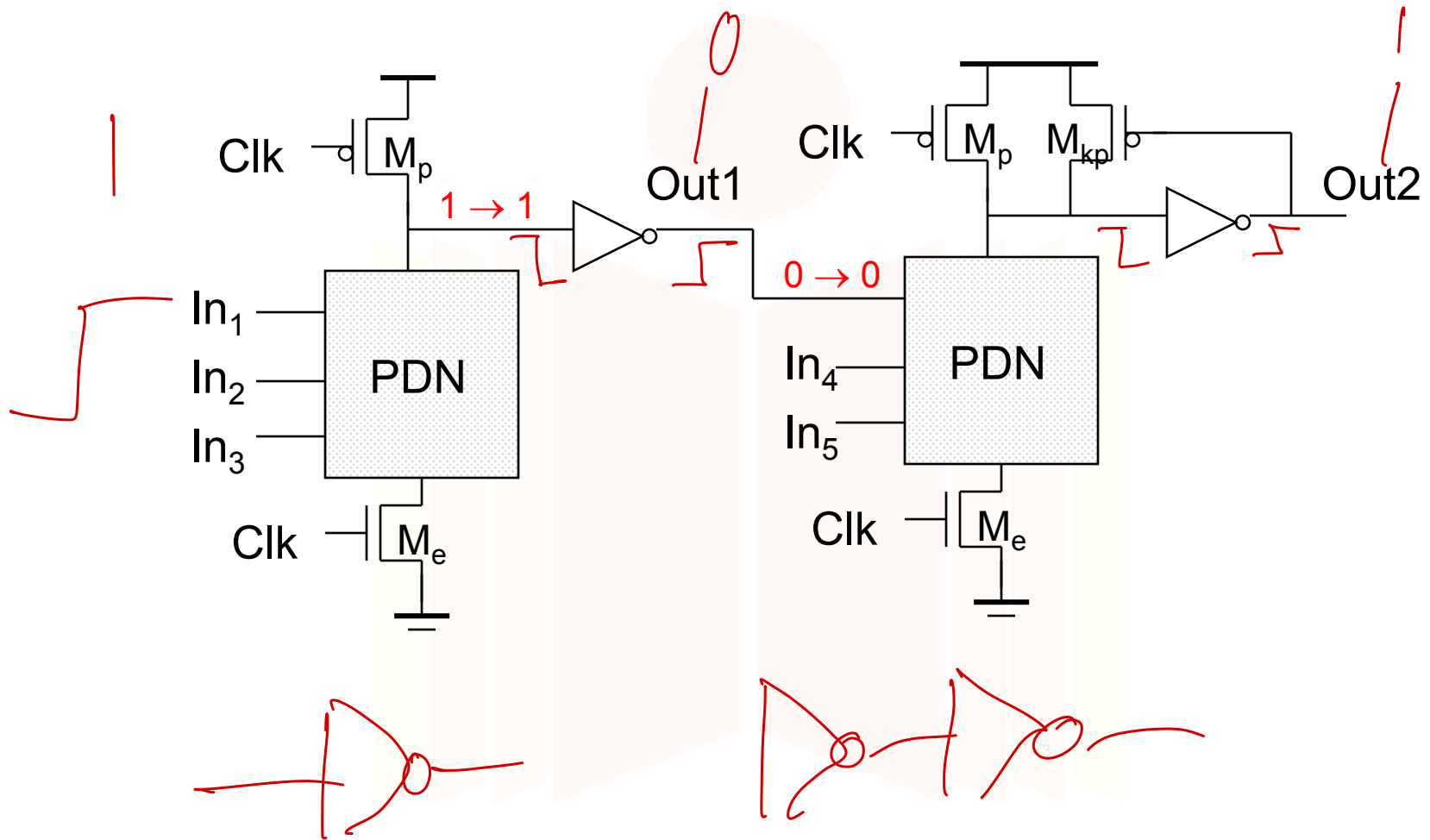


Why Domino?

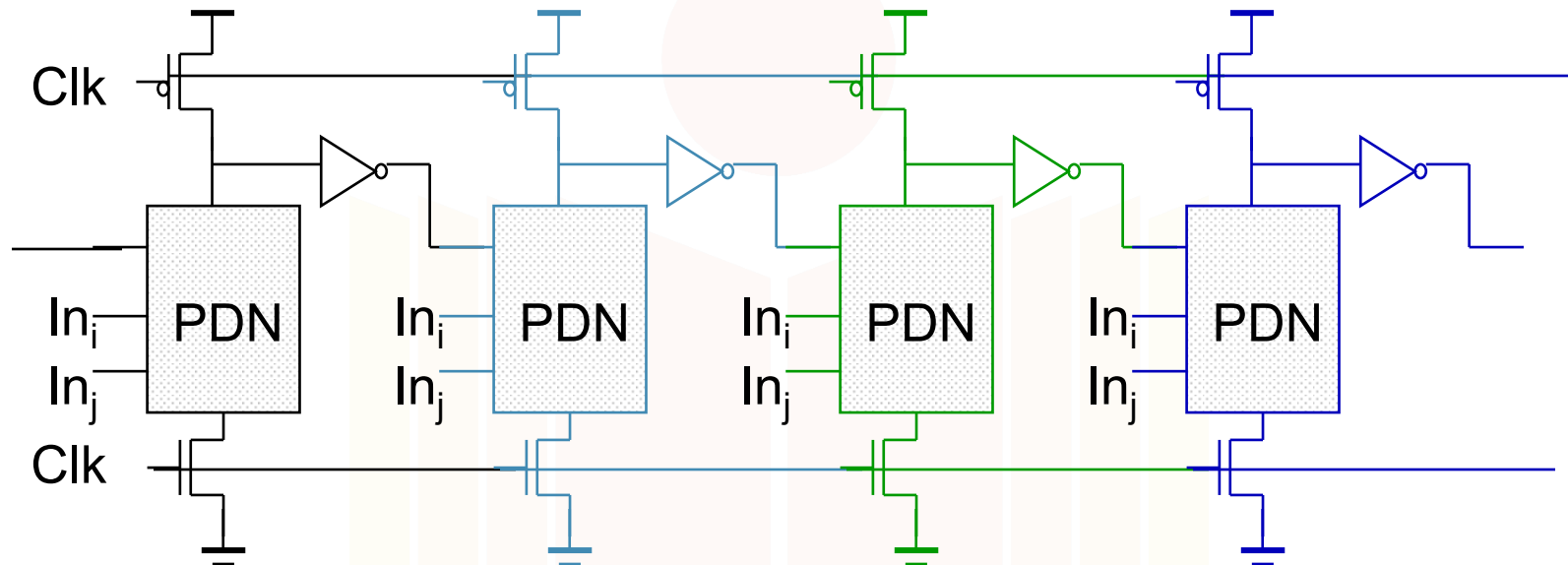

Properties of Domino Logic

- ❑ Only non-inverting logic can be implemented
- ❑ Very high speed
 - dynamic inverter can be skewed, only L-H transition
 - Input capacitance reduced – smaller logical effort

NORA Logic

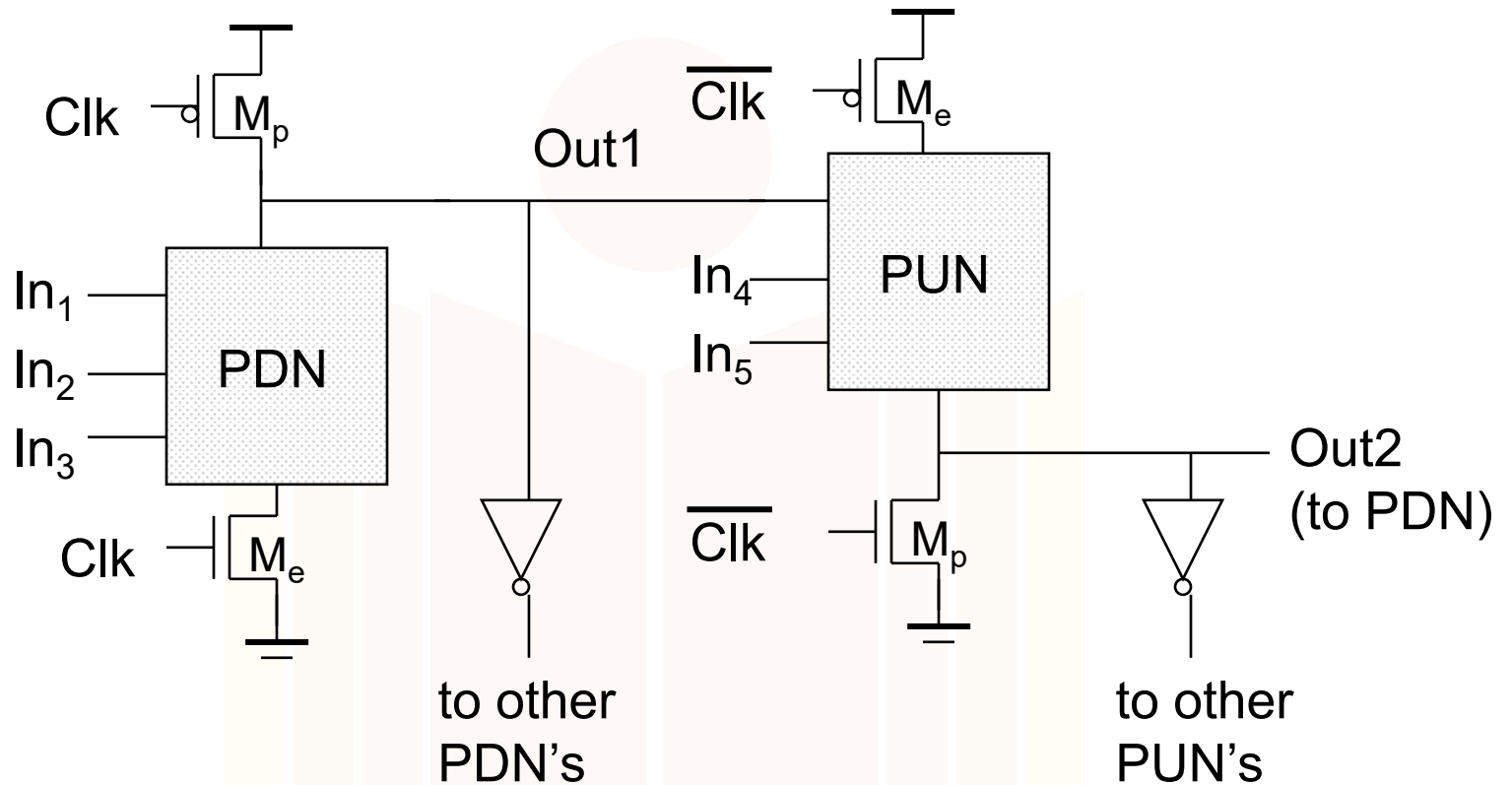

WARNING: Very sensitive to noise!