




EE5153: Introduction to VLSI Design


Implementation of Arithmetic in VLSI

Acknowledgement: Material primarily from textbook and lecture slides for Rabaey et. al. Digital Integrated Circuits, 2nd Edition (2002).

A Generic Digital Processor

 

Control

 

Bit sliced design for datapath

- Arithmetic Unit
 - Datapath (adder, multiplier, shifter, comparator, etc)
- Memory
 - RAM, ROM, Buffers, Shift Registers
- Control
 - Finite State Machine (PLA, random logic)
 - Counters
- Interconnect
 - Switches
 - Bus




Adders

- ❑ Half Adder
- ❑ Full Adder
- ❑ Ripple Carry Adder



Full Adder

 

$$A \oplus B \oplus C$$

$$S = ? \quad ABC + A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C$$

$$C_{out} = ? \quad AB + BC + CA$$

| A | B | Cin | Sum | Cout |
|---|---|-----|-----|------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |




Direct CMOS Implementation of Full Adder

$$S = ABC_i + \overline{C_{out}}(A + B + C_i)$$

$$C_{out} = AB + BC_i + AC_i$$

LE of $C_i = ?$


LE of A = ?

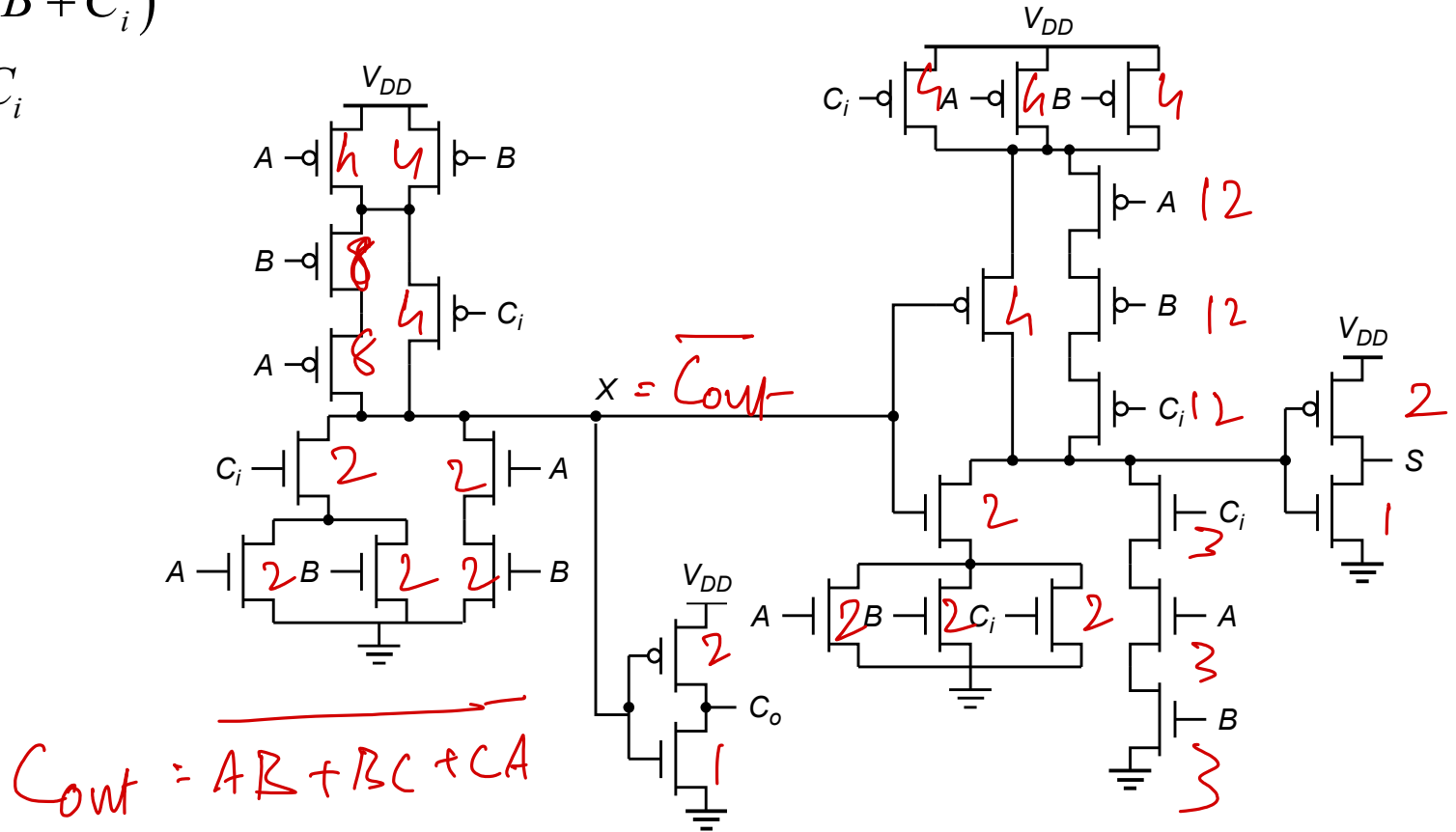

28 Transistors!!



Ripple Carry Adder (RCA)

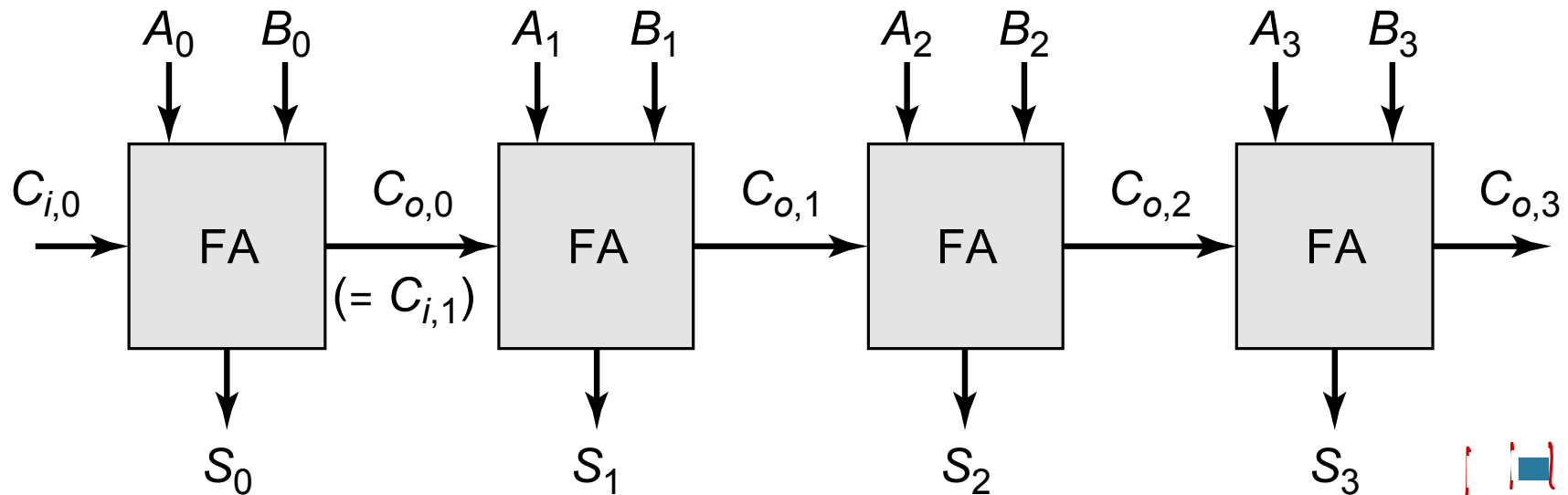

Handwritten binary addition example:

$$\begin{array}{r} 1111 \\ 0001 \\ \hline 10000 \end{array}$$

Worst case delay linear with the number of bits


$$t_d = O(N)$$

$$t_{\text{adder}} = (N-1)t_{\text{carry}} + t_{\text{sum}}$$

Goal: Make the fastest possible carry path circuit



Inversion Property

 


$$\overline{S}(A, B, C_i) = S(\overline{A}, \overline{B}, \overline{C_i})$$

$$\overline{C}(A, B, C_i) = C(\overline{A}, \overline{B}, \overline{C_i})$$



 Minimize Critical Path by Reducing Inverting Stages




Here, FA stands for full adder without the inverter in carry path



The Mirror Adder

$$S = ABC + \overline{C}_{out} (A \oplus B \oplus C)$$


$$C = AB \oplus BC \oplus CA$$

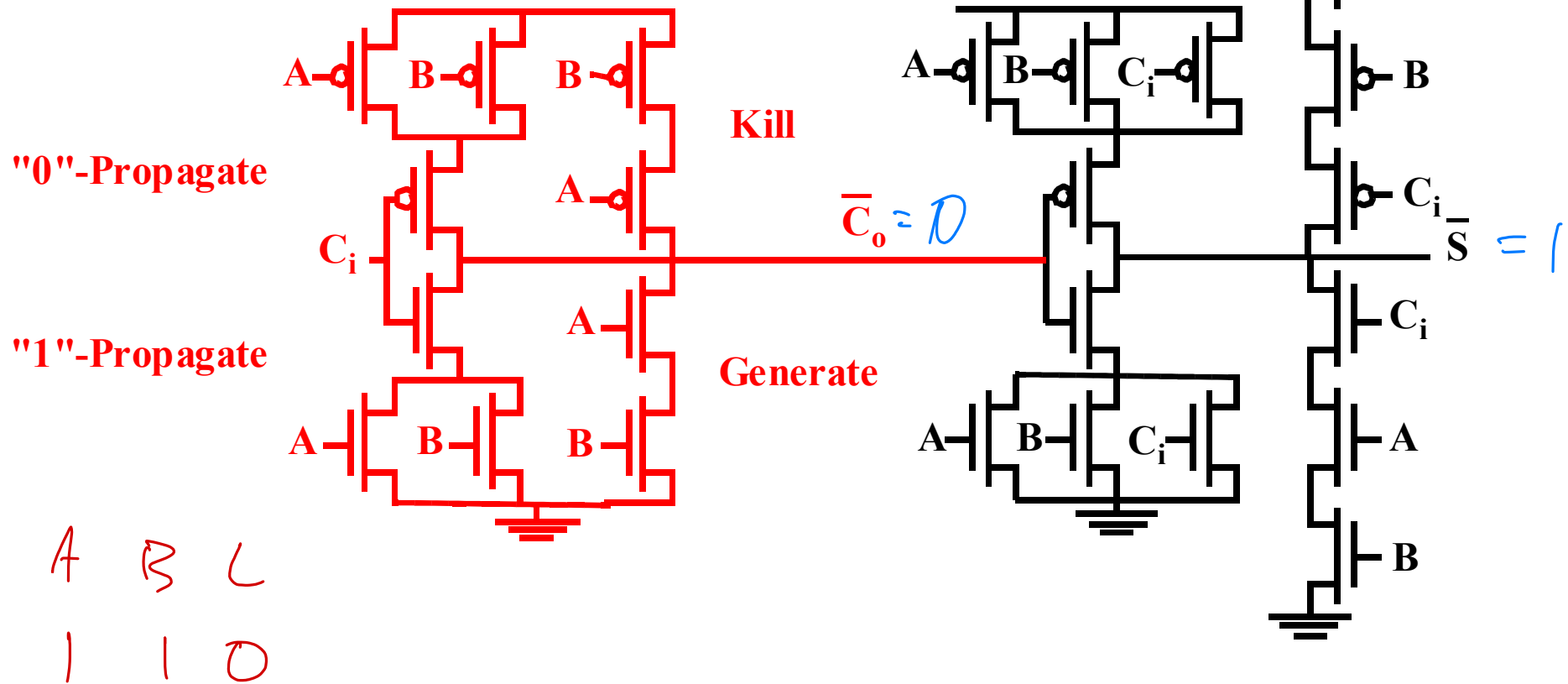


How to size the adder to optimize the delay in the carry chain?



Mirror Adder – The stick diagram

 

 

$N = 21, 101$

