

Analog Lab
Experiment 7: Buck Converter

Name- Pushkal Mishra
Roll- EE20BTECH11042

1. To design a Buck converter with the following specifications

Input Supply: $V_{sup} = 5V$

Output Voltage: $V_{O1, avg} = 2.5V$


Switching Frequency: $f_s = 1MHz$

Load: $R_L = 100\Omega$ resistor with $I_o = 100mA$ current source

Output Ripple Voltage $\leq 10mV$

Quality factor: $Q = 3$

Circuit Used

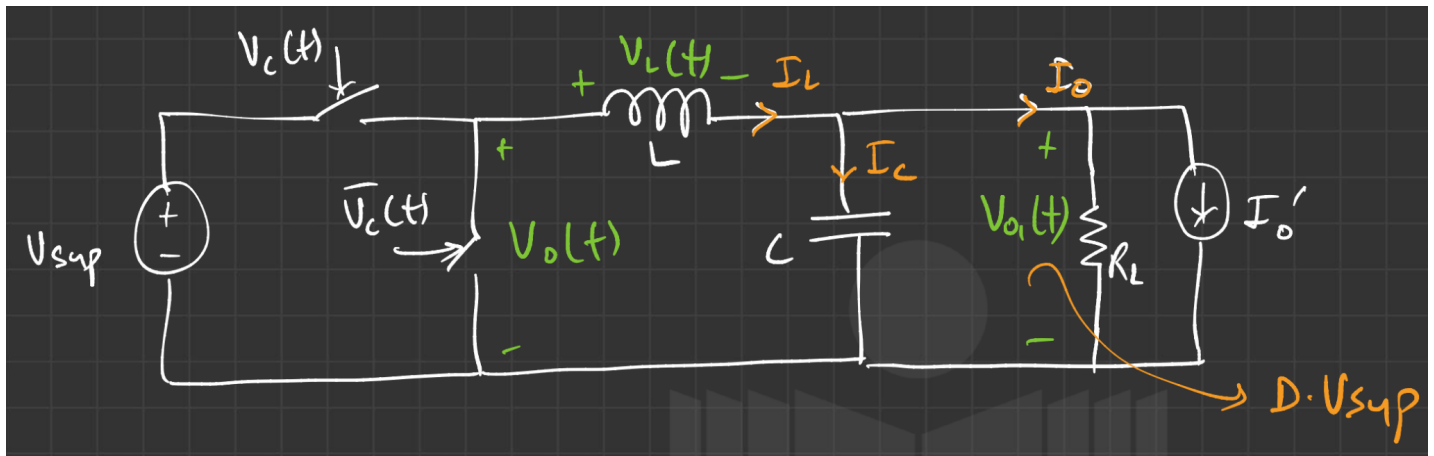

Now the average voltage of V_{O1} is DV_{sup} where D is duty cycle and V_{sup} is $5V$. Given the average of V_{O1} as $2.5V$, we get the duty cycle D as 0.5

Relation between peak-to-peak voltage of V_{O1} is-

$$V_{O1, PP} = \frac{(1-D)DV_{sup}}{8LCf_s^2}$$

Using the given condition that $V_{O1, PP} \leq 10mV$ and substituting values of $D(0.5)$, $f_s(1MHz)$ and $V_{sup}(5V)$ we get-

$$LC \geq \frac{5 \times 10^{-10}}{32} \rightarrow \text{Eq 1}$$

Quality factor for LC circuit is given as-

$$Q = R_L \sqrt{\frac{C}{L}}$$

Substituting values of $Q(3)$ and $R_L(100\Omega)$ we get-


$$\frac{C}{L} = 9 \times 10^{-4} \rightarrow \text{Eq 2}$$

Taking equality in equation 1 and dividing with equation 2 we get L as 0.1317 mH and C as 118.59 nF .

In this experiment I have taken L as 0.13 mH and C as 118.6 nF .

All these formulas and circuits are from Analog Electronics lecture 18 and 19.


Implementation in LTSpice

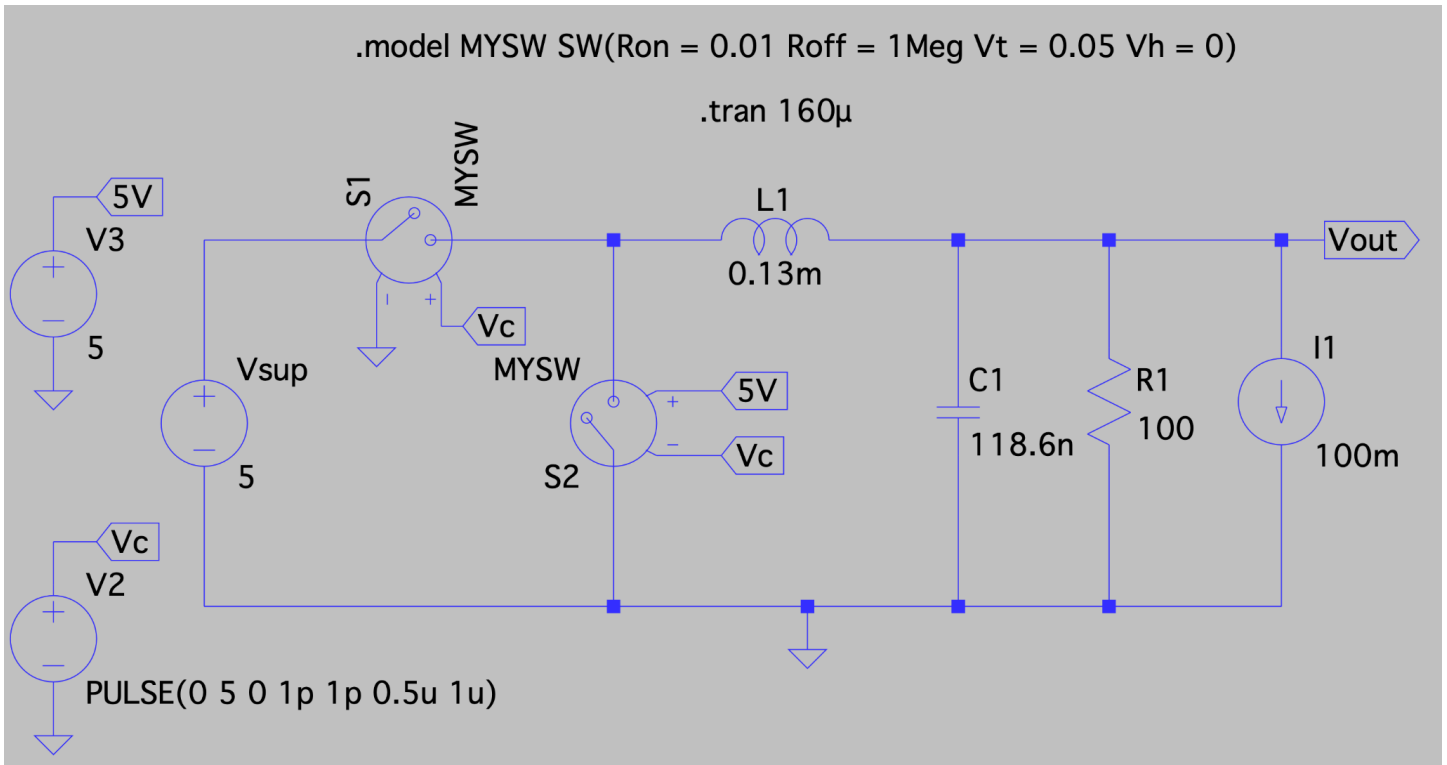


Here we used the voltage controlled switch to implement the switching mechanism. The specifications of the switch are as follows: $R_{on} = 0.01\Omega$, $R_{off} = 1\text{M}\Omega$, $V_T = 0.05\text{V}$ and $V_H = 0\text{V}$. A low value of R_{on} and high value of R_{off} helps in keeping the switching mechanism to near ideal condition.

In S1, V_C is compared to ground, i.e. $V_C - 0 = V_C$ and in S2, V_C is compared to 5V, i.e. $5 - V_C = \overline{V_C}$.


Transient Simulation

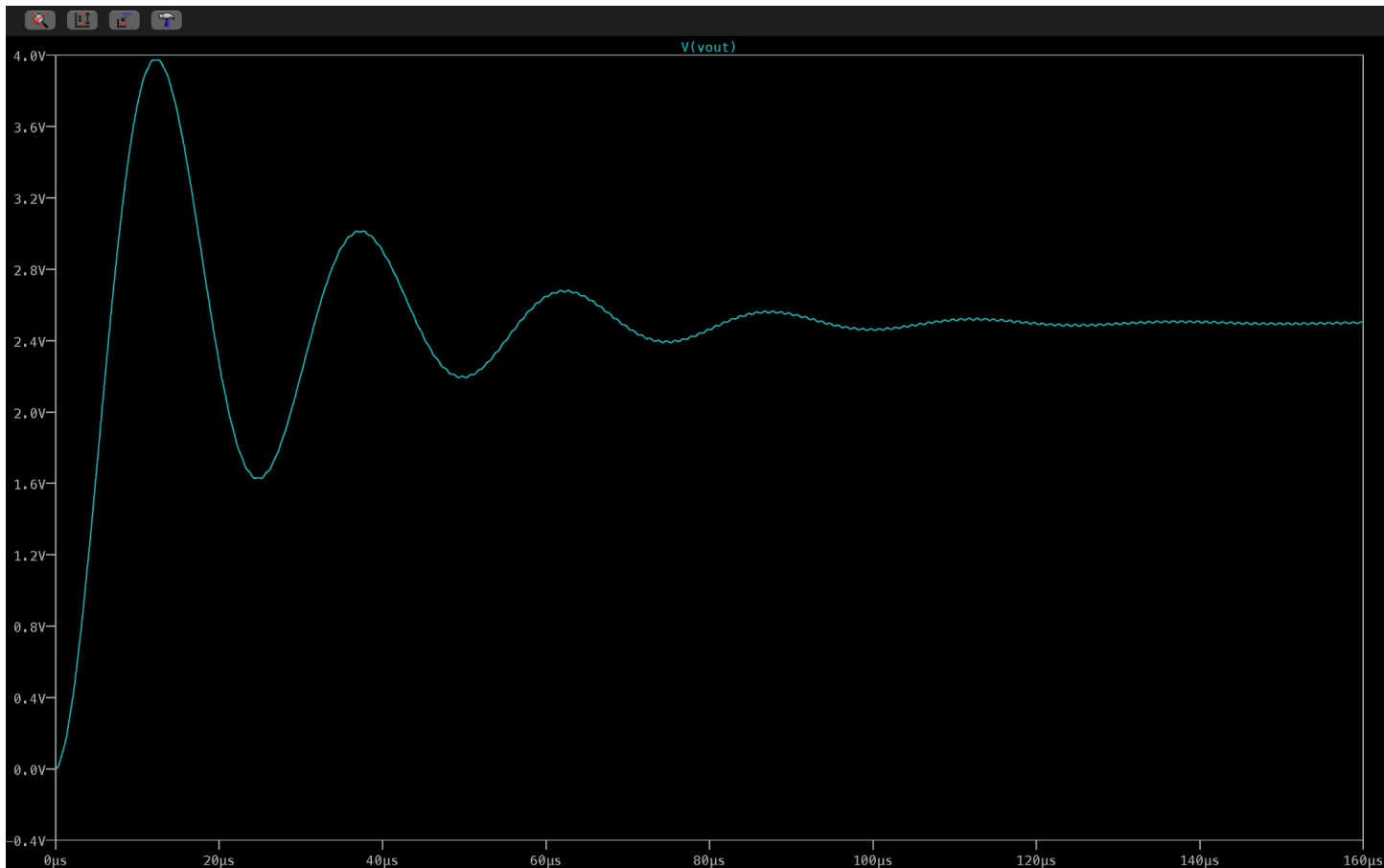

Steady State Simulation

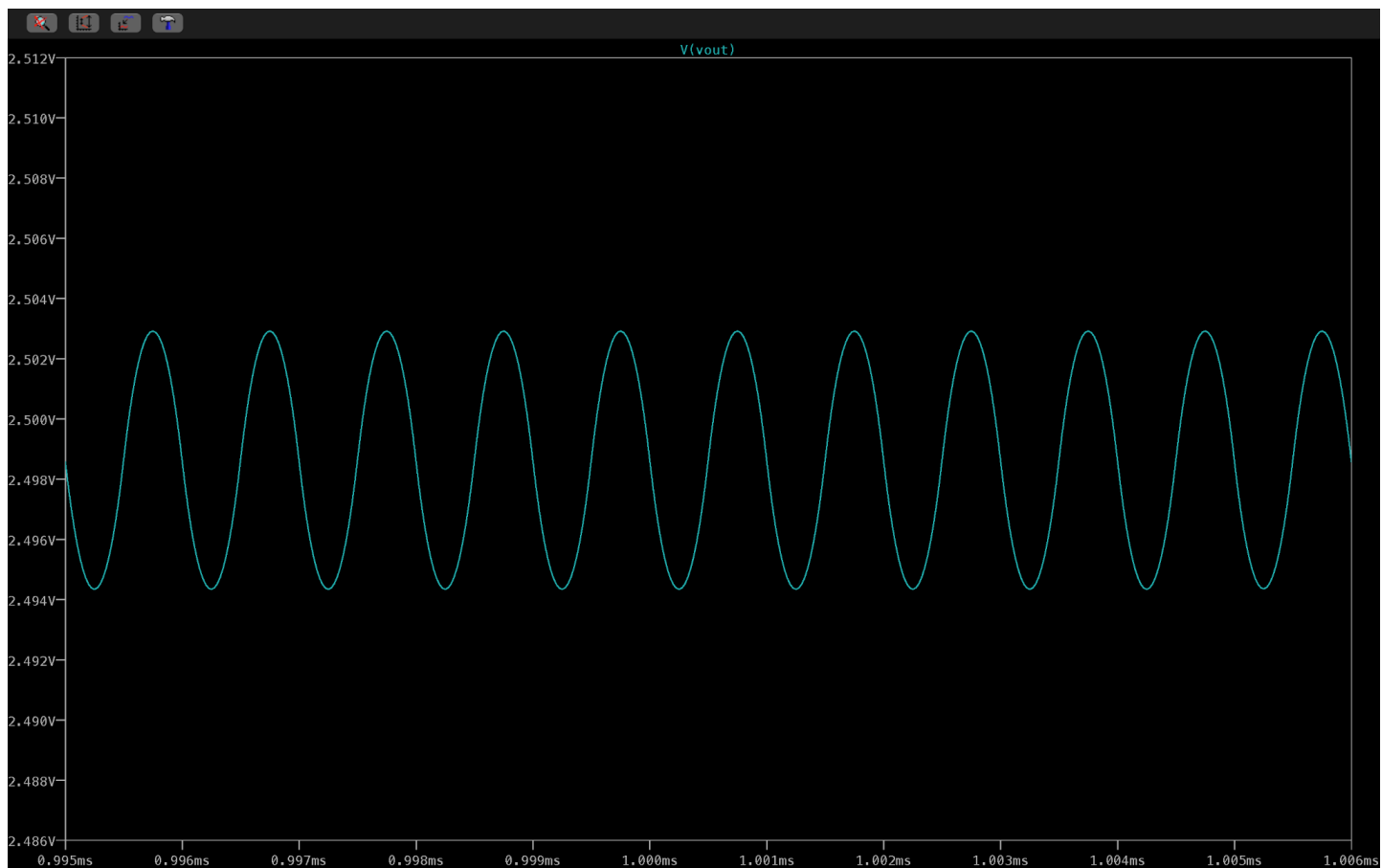

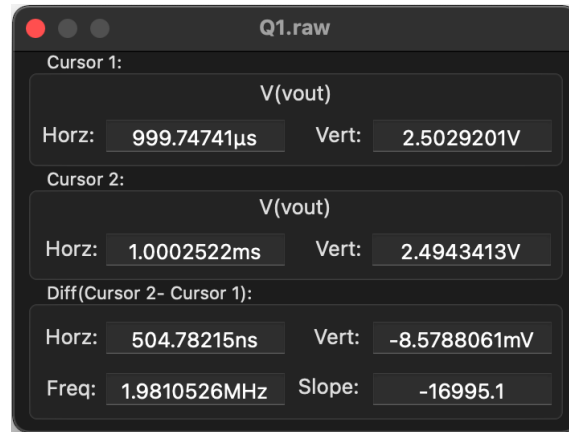Finding Ripple Voltage using Cursor in LTSpice



From the above measurements, ripple voltage is $8.57 \text{ mV} \leq 10 \text{ mV}$.

2. Some observations

2.1 The ripple voltage is as expected.

2.2 The transient response is similar to an under-damped system.

2.3 We can control the ripple voltage by varying L and C.

2.4 The above circuit acts as a DC to DC step down voltage transformer.