

① Design a buck-converter to meet the following requirements:—

- * Input supply = 5V, Output supply = 2.5V
- * Switching freq. = 1MHz
- * Load \rightarrow 100Ω in parallel with 100mA
- * Output voltage ripple $\leq 10\text{mV}$ peak-to-peak
- * Quality factor of L-C filter = 3

Submit the following:—

- (a) Hand calculation to find the component values.
- (b) Simulation test-bench in LTspice.
- (c) Transient simulation result showing initial transient in the output voltage.
- (d) Steady-state output voltage indicating ripple.