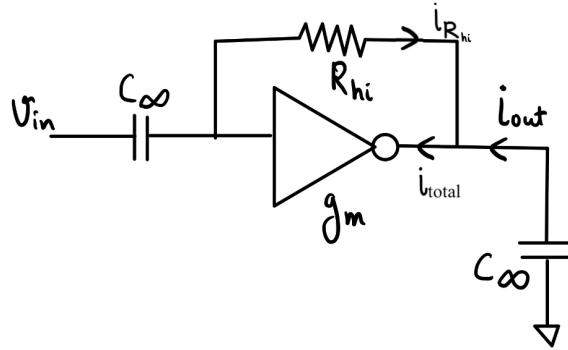


**Analog Lab**  
**Experiment 2:  $g_m$ -C Filter**

Name- Pushkal Mishra  
Roll- EE20BTECH11042

**1. Calculating value of  $R_{hi}$**



From the circuit, by applying KCL we get-

$$i_{total} = i_{out} + i_{R_{hi}}$$

A capacitor with infinite capacitance will act as a short circuit since the time constant is infinite so the capacitor plates will never rise from 0V. So the voltages across the inverter are  $v_{in}$  and 0V.

Therefore-

$$i_{total} = g_m v_{in} = i_{out} + \frac{v_{in} - 0}{R_{hi}}$$

$$g_m = \frac{i_{out}}{v_{in}} + \frac{1}{R_{hi}}$$

From the question-

$$\frac{i_{out}}{v_{in}} = 0.99g_m$$

So we get-

$$R_{hi} = \frac{100}{g_m} = \frac{100}{1.81826 \text{ mmho}}$$

$$R_{hi} = 55 \text{ k}\Omega$$

We are neglecting  $r_o$  here as it is in the order of  $M\Omega$ .


## 2. Designing a $g_m$ -C filter with

Resonant Frequency:  $\omega_0 = 10\text{kHz}$

Supply Voltage:  $V_{DD} = 6\text{V}$

Quality Factor:  $Q = 2$

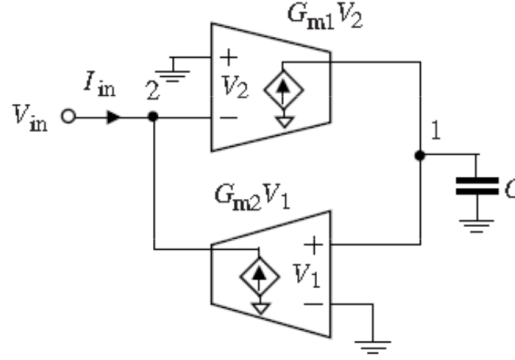First we need to find the inductance based on  $g_m$  and  $C_2$ .



Reference [link](#)

In the circuit we can observe that the current entering the capacitor is  $-g_{m1}V_2$  (due to the polarity of  $V_2$ ). Also the V-I relation for capacitor in s domain is-

$$(0 - V_1) \times sC = i_{\text{capacitor}} = g_{m1}V_2$$

Therefore we get-

$$V_1 = -\frac{g_{m1}V_2}{sC}$$

Also observe that -

$$I_{in} = -g_{m2}V_1 = \frac{g_{m1}g_{m2}V_2}{sC}$$

Rearranging the terms we get-

$$V_{in} = V_2 = \frac{sC}{g_{m1}g_{m2}}I_{in}$$

The above equation suggests that the setup acts as an inductor with impedance equal to  $\frac{sC}{g_{m1}g_{m2}}$  (like an inductor).

Since  $g_{m1}$  and  $g_{m2}$  are equal in the given question, the equivalent impedance becomes equal to  $\frac{sC}{g_m^2}$ .

Given resonant frequency as 10kHz, so

$$f_R = 10kHz = \frac{\omega_0}{2\pi}$$

$$\omega_0 = 62.832 \text{ krad/s}$$

Now as we are implementing resistance R with inverter, so resistance will be


$$R = \frac{1}{g_m} = 549.98\Omega$$

$$Q = 2 = \frac{\omega_0 C_1}{g_m} \Rightarrow C_1 = 57.876 \text{ nF}$$


$$\omega_0 = 62.832 \times 10^3 = \frac{g_m}{\sqrt{C_1 C_2}} \Rightarrow C_2 = 14.469 \text{ nF}$$

These formulas are from  
in class derivation  
for second order parallel  
RLC filters


Circuit implementation in LTSpice-

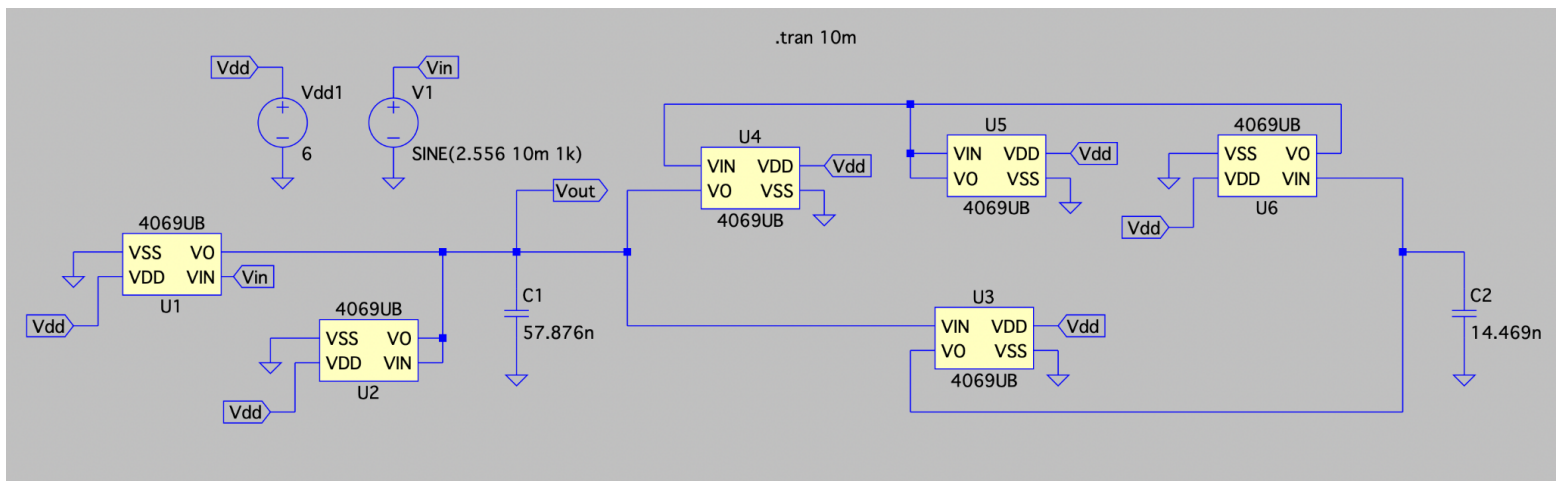


Output plot for input frequency of 1kHz-

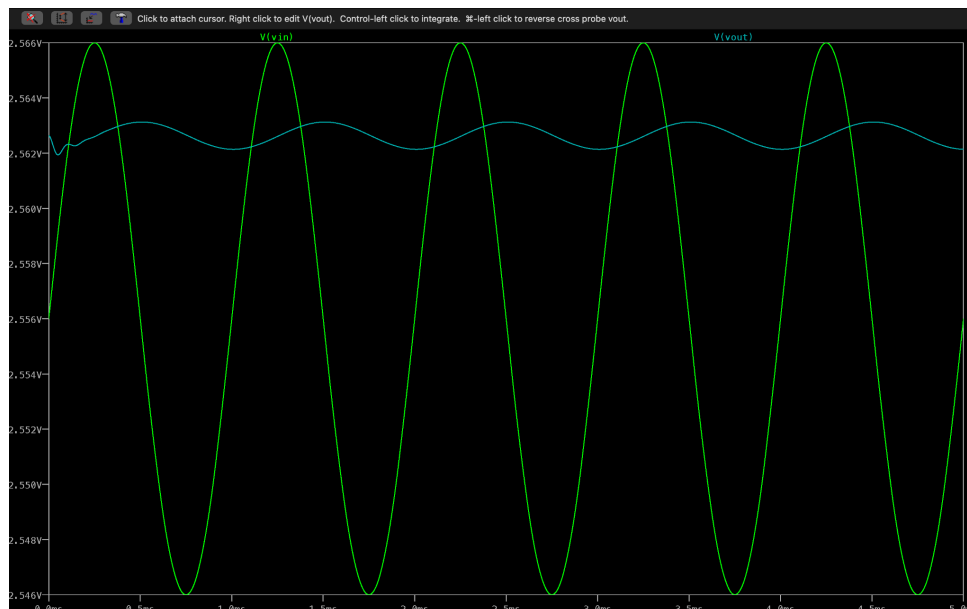

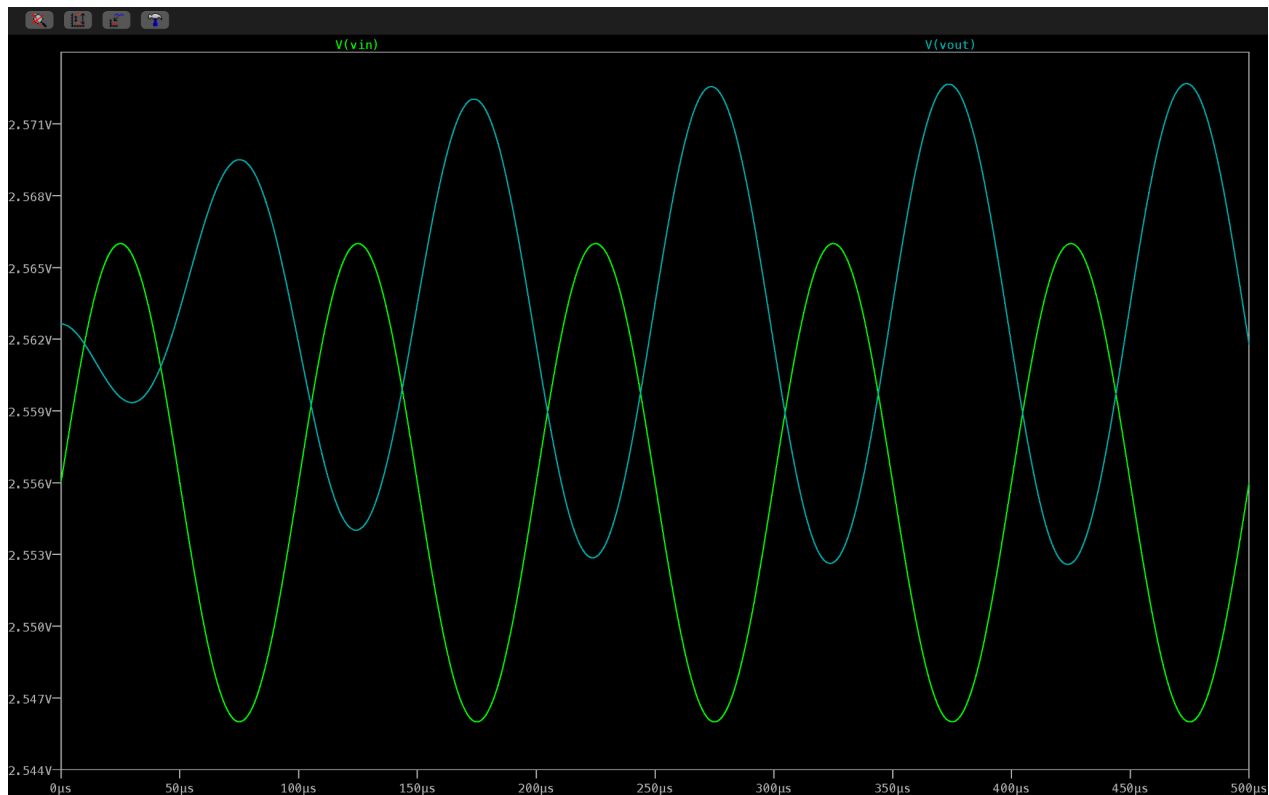Output plot for input frequency of 10kHz-



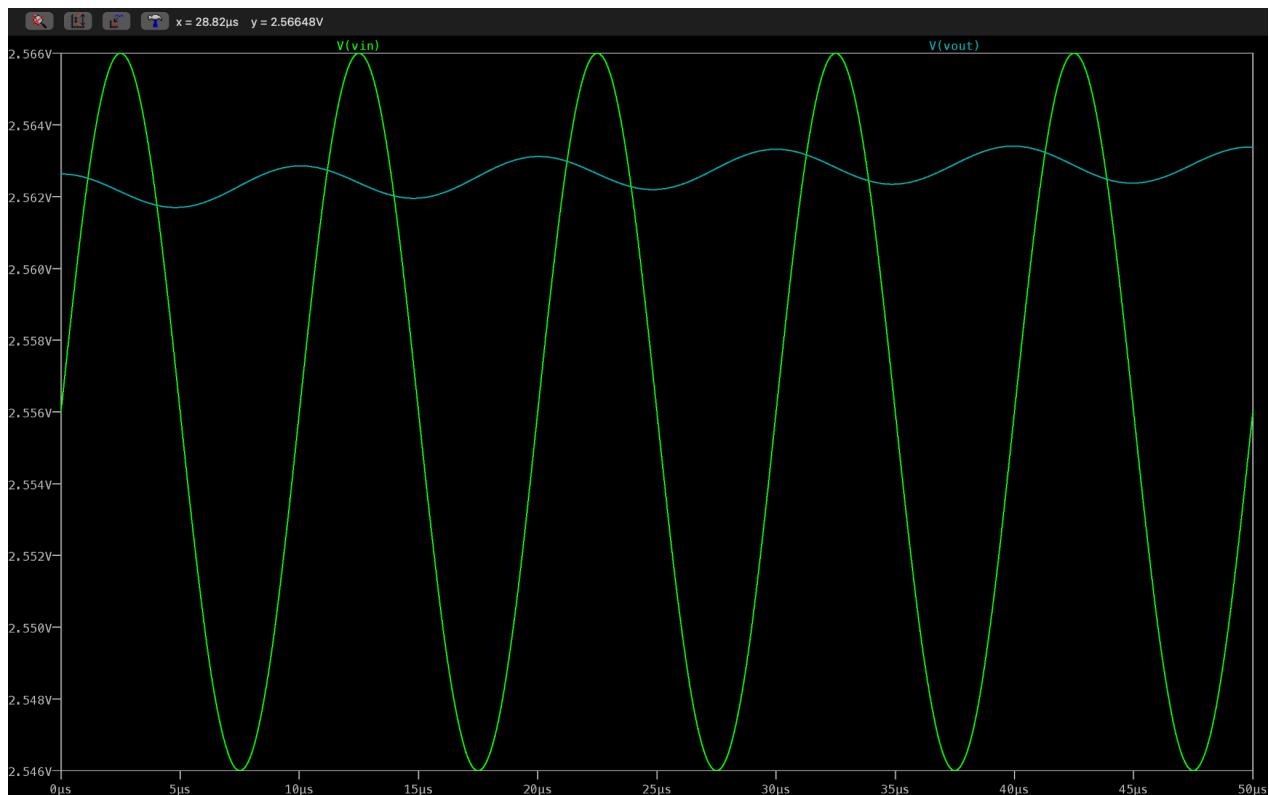Output plot for input frequency of 100kHz-




Clearly from the output plots, the filter damps the input signal at frequencies of 1kHz and 100kHz but does not damp the signal with frequency 10kHz. So we can conclude that the filter acts as a band pass filter.


Also observe that the phase difference between input and output signals are  $180^\circ$  at frequency 10kHz.

### 3. Bode plot by varying $V_{DD}$ from 5V to 9V

Circuit used-

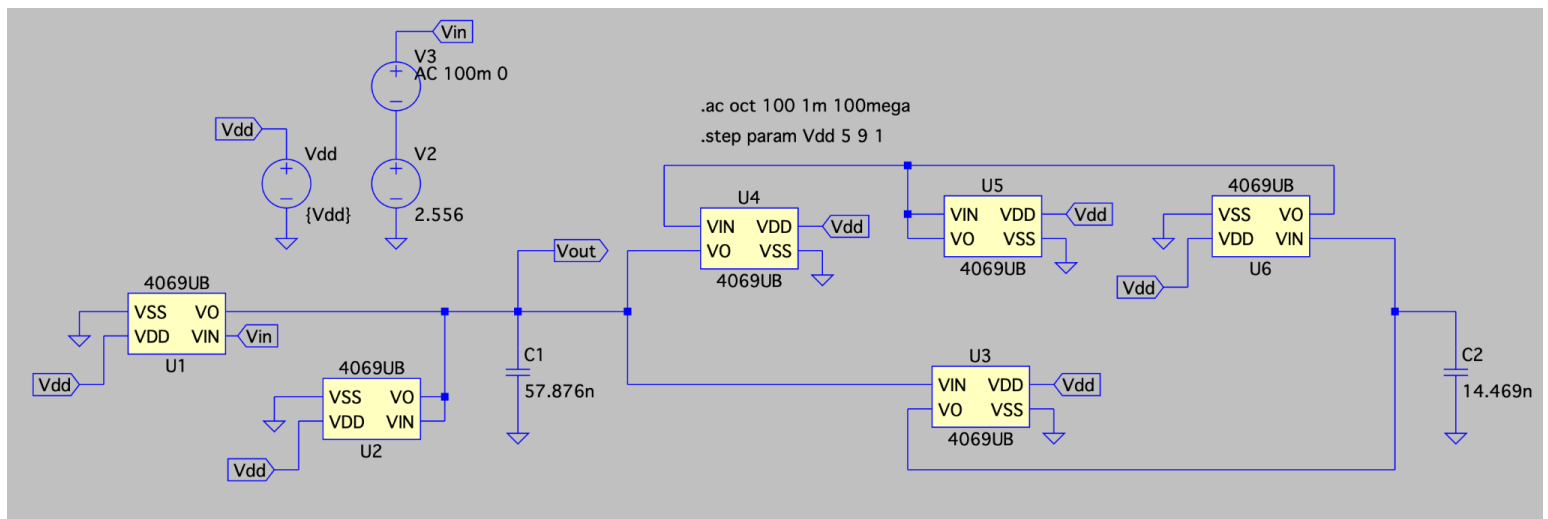

Bode plot obtained-

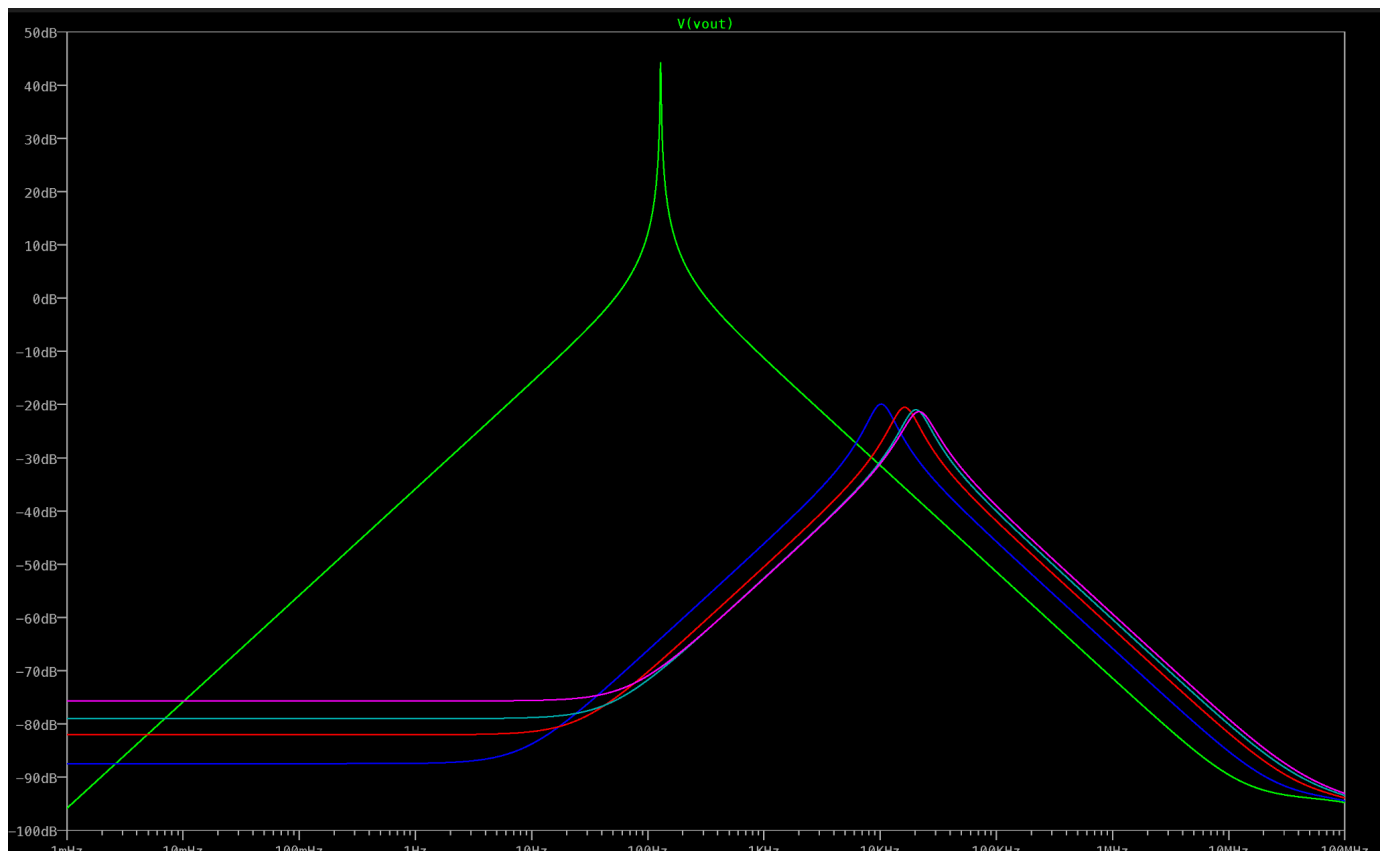

As concluded from the previous experiment, when  $V_{DD}$  equals 5V the inverter acts as a logic device and so the output voltage either stays at 0 or  $V_{DD}$ . In the bode plot, the green line indicates at  $V_{DD}$  equal to 5V.

From the previous experiment, value of  $g_m$  came out to be

$$g_m = \beta_n (V_{GS} - V_{THn})(1 + \lambda_n V_{DS}) + \beta_p (V_{SG} - |V_{THp}|)(1 + \lambda_p V_{SD})$$

Clearly  $g_m$  increases as  $V_{DD}$  increases (from the above equation) which is also observed in the right shifting of the plot as  $V_{DD}$  increases since the natural frequency  $\omega_0$  is directly proportional to  $g_m$ . Also from the graph the Q factor does not appear to change much and even from the equations in 2, Q does not depend on  $g_m$ .

One application of this phenomenon is that we can change  $V_{DD}$  to set the resonant frequency of a second order band pass filter and can be used to apply in communication devices.

*(The UI is different as I am using a Mac. Also I was unable to find the legend option for the bode plot as it is not available on M1 mac.)*