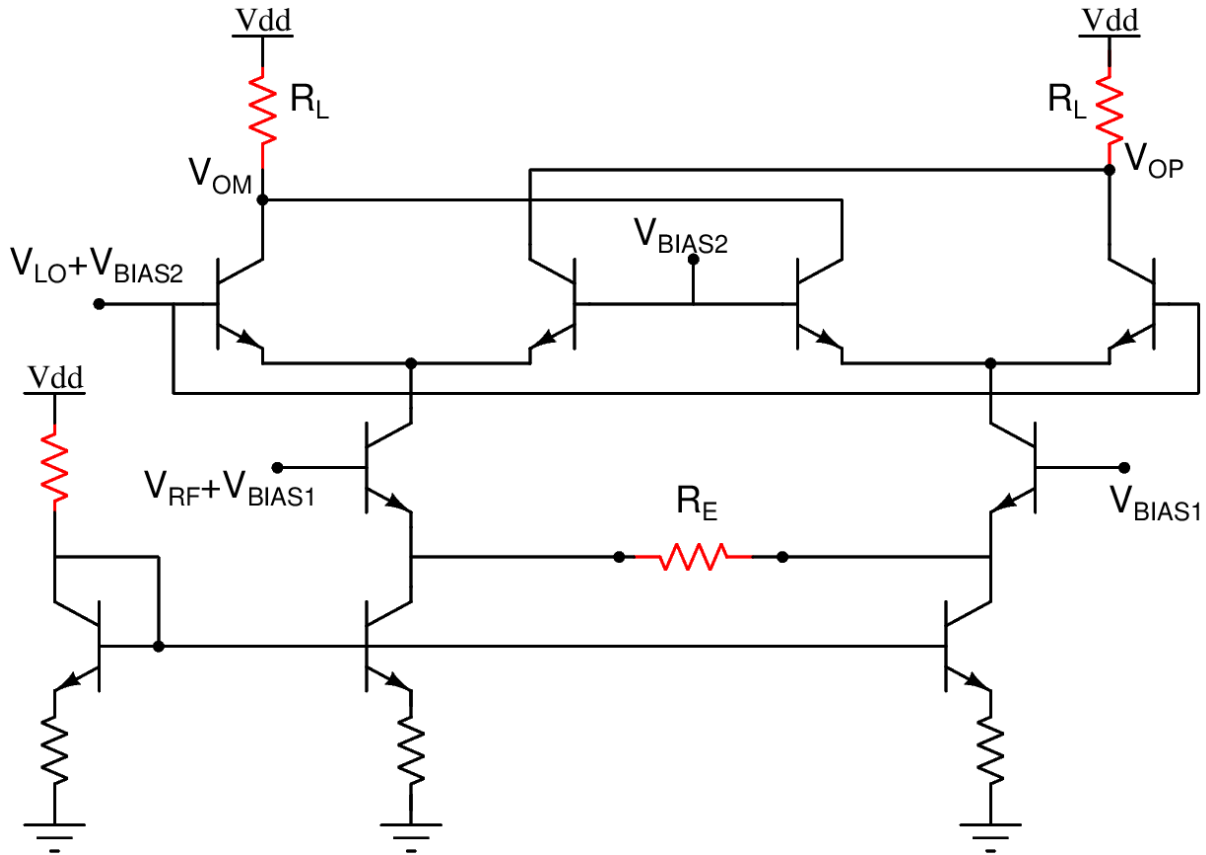


**Experiment 11: Double balanced mixer**

1. Below is the schematic of a double-balanced mixer present in MC1496 IC:



Components in RED are external to the IC.

- Input signal frequency ( $V_{RF}$ ): 11 kHz
- $V_{LO}$ : 10 kHz output from the oscillator designed in Exp. 5


Plot transient simulation result and FFT of the output  $V_O = V_{OP} - V_{OM}$ . Connect appropriate value of capacitors across  $R_L$  to filter out undesired components. Generate bias voltages from the supply. Connect bypass capacitors for the bias voltages.

2. Differential output of the mixer can be converted into single-ended by using the following circuit:

What is the expression for the single-ended output in terms of supply voltage,  $i_1$ ,  $i_2$  and  $R_L$ ?

Use the signal specs given in the previous problem and perform the following

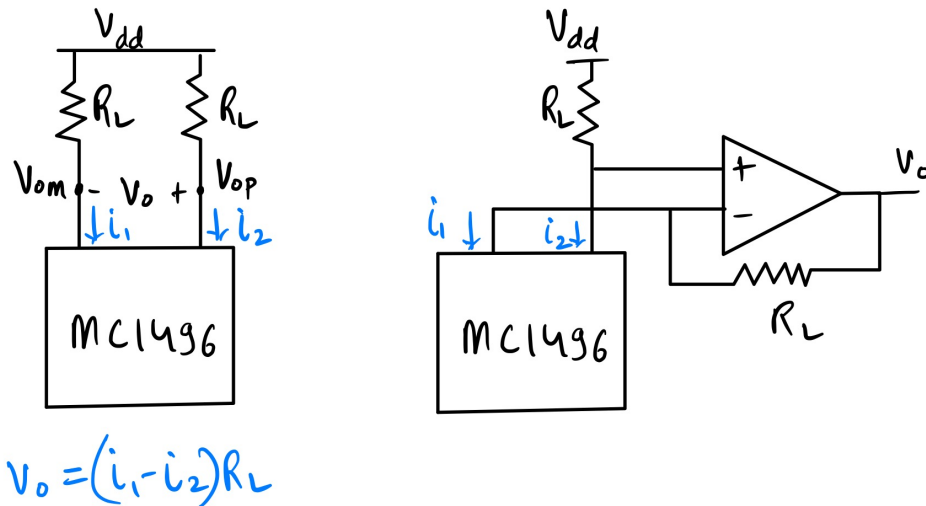- Plot single-ended output. (Transient and FFT)



- Apply only  $V_{RF}$  and  $V_{LO}$  one at a time and make your observation regarding the output.

#### CAD info:

- LF347 <https://www.ti.com/product/LF347#product-details>
- MC1496 <https://www.onsemi.com/products/audio-video-assp/audio-assp/mc1496>
- PSPICE models can be used in LTspice using this procedure: <https://www.analog.com/en/technical-articles/ltspice-simple-steps-to-import-third-party-models.html>

#### Submit the following:

- Testbench snapshot, output plots
- Hand calculation
- Any unusual observation along-with comments