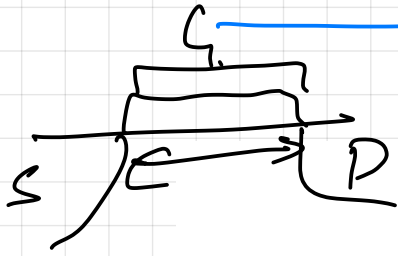



Lecture 2: NMOS Inverter

02/08/2022




$L < 1 \mu m$





$L = 0.25 \mu m$

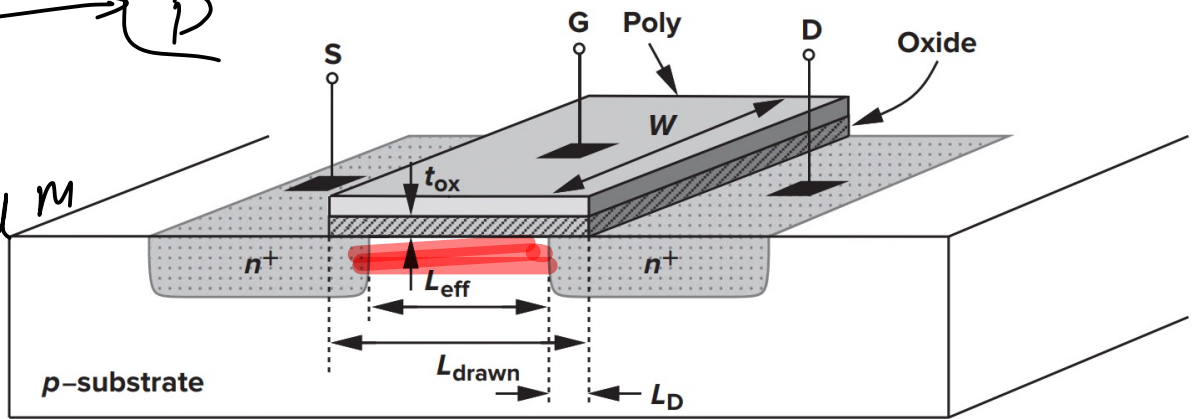

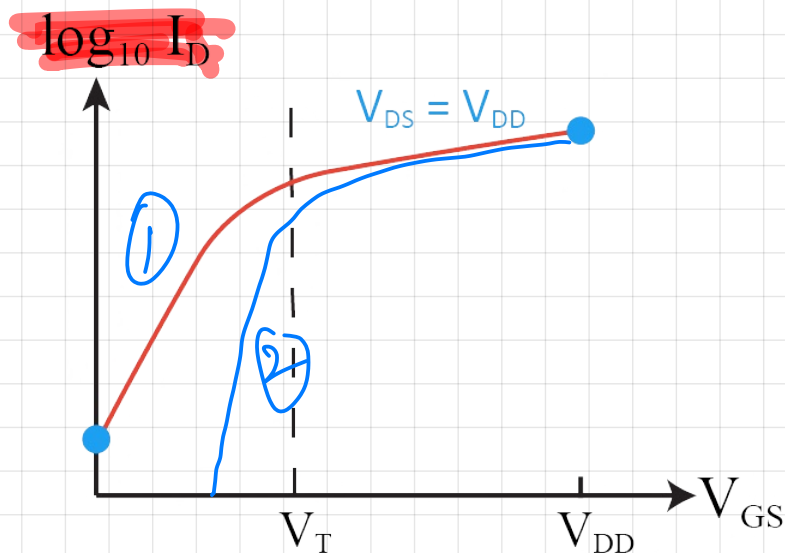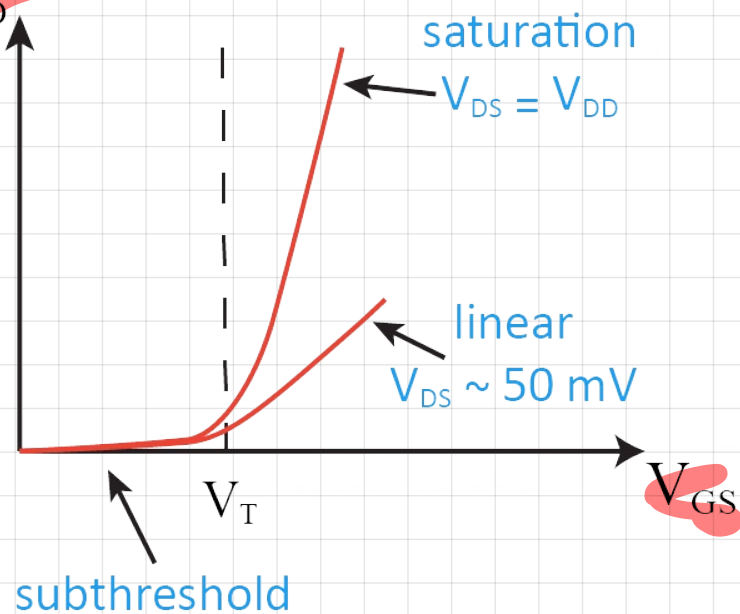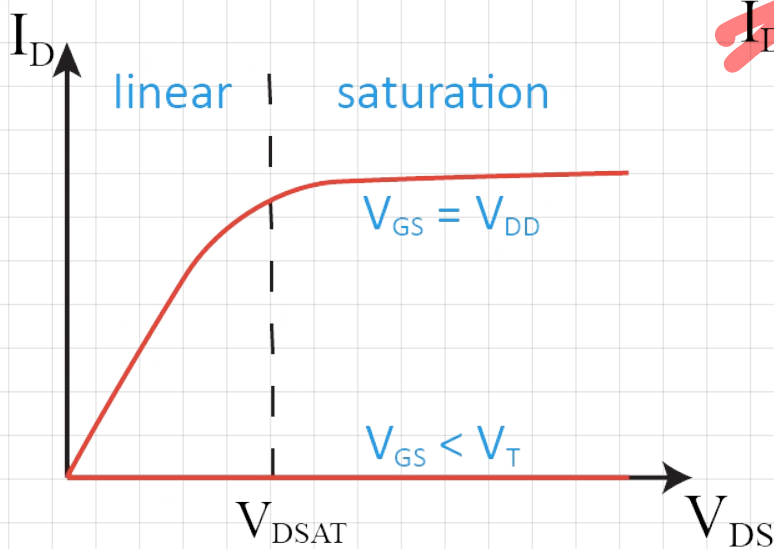
$$I_D = \mu C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$



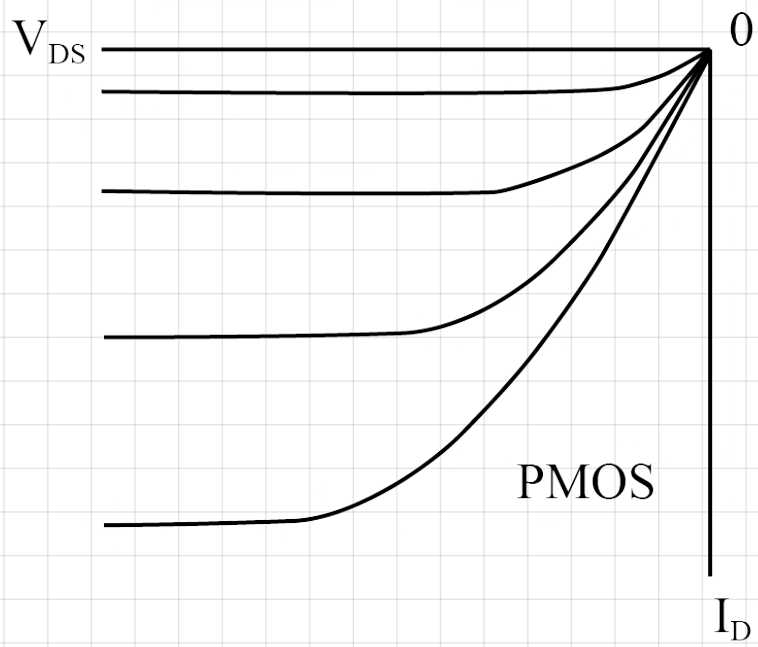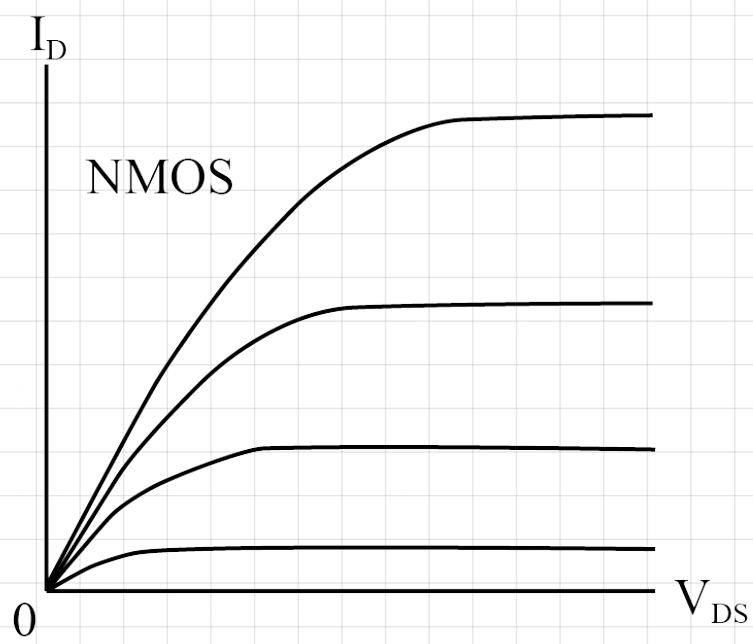


Logic Inverter

I_n	O_{ut}
0	1
1	0

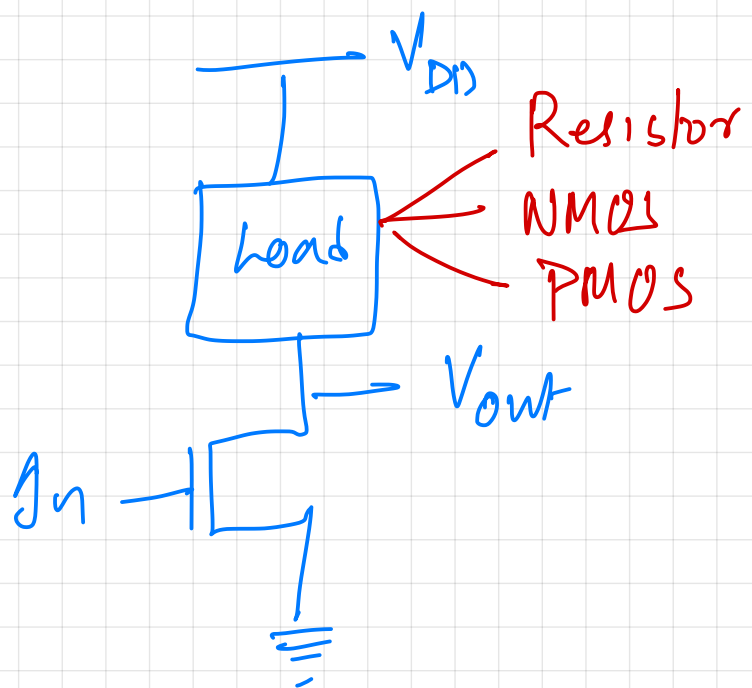


$V_{in} = V_{DD}$ $V_{out} = ?$ 0

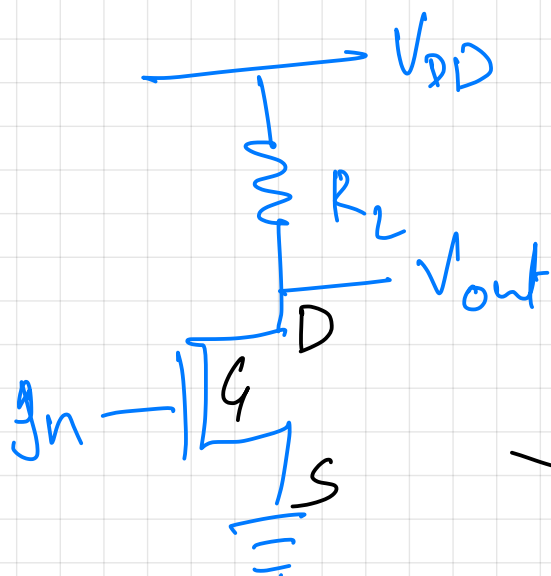

$V_{GS} = V_{DD} > V_{Th}$

$V_{in} = 0$


$V_{in} = V_{DD}$

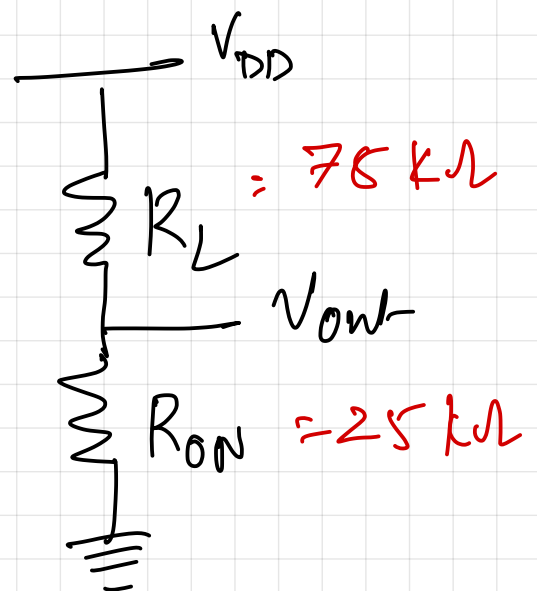

$R_L = 75 \text{ k}\Omega$

V_{out}

$R_{on} = 25 \text{ k}\Omega$


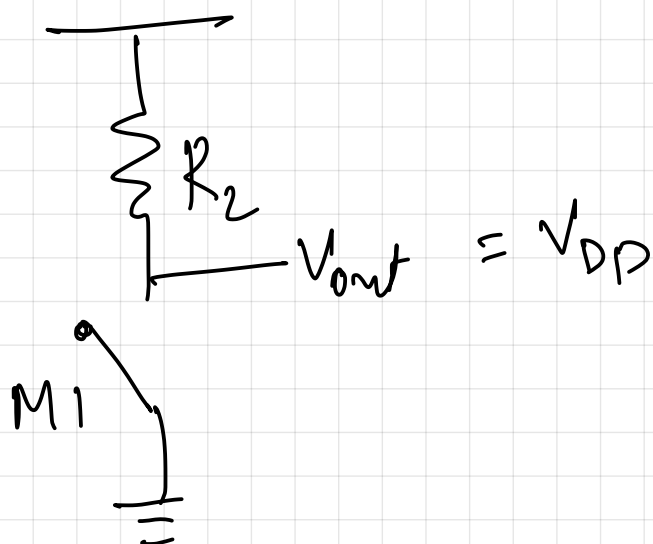


$V_{out} = V_{DD}$

$V_{out} = \frac{R_{on}}{R_{on} + R_{out}}$

0.25 V

Voltage Transfer Characteristic (VTC)

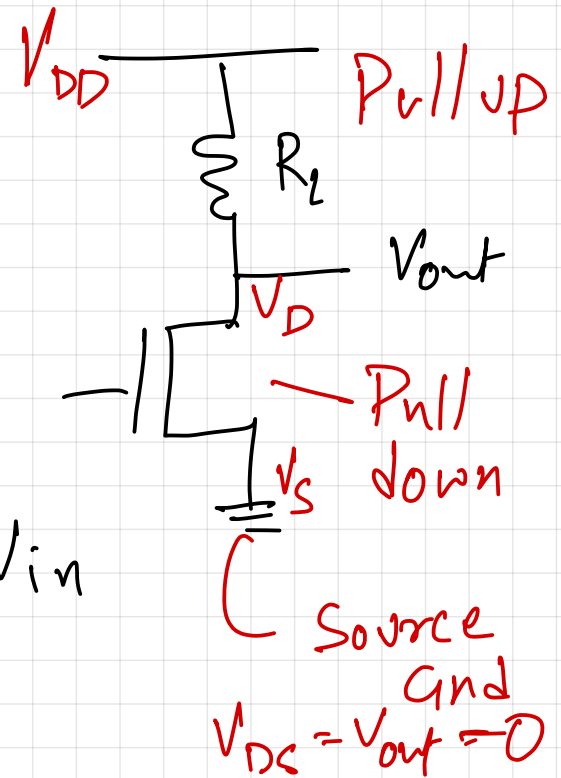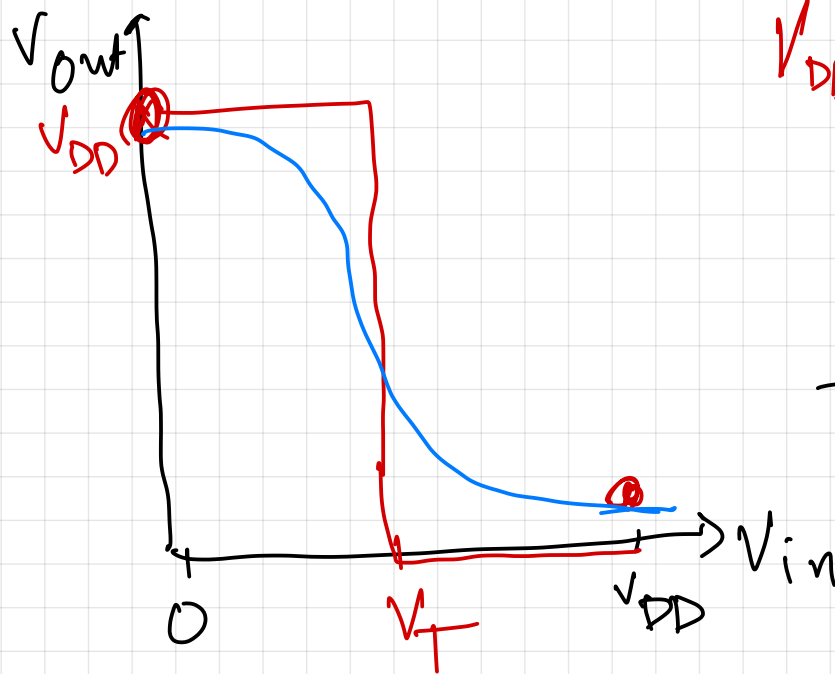


$$\frac{V_{DD} - V_{out}}{R_L} = \mu C_{ox} \frac{W}{L} \left[(V_{gs} - V_T) V_{out} - \frac{V_{out}^2}{2} \right]$$

$0 \rightarrow V_{DD}$

V_{OH} : Nominal high voltage

$$5V \rightarrow 3.3V \rightarrow 2.5V - 1.8V \rightarrow 1.1V$$

V_{OL} : Nominal low voltage

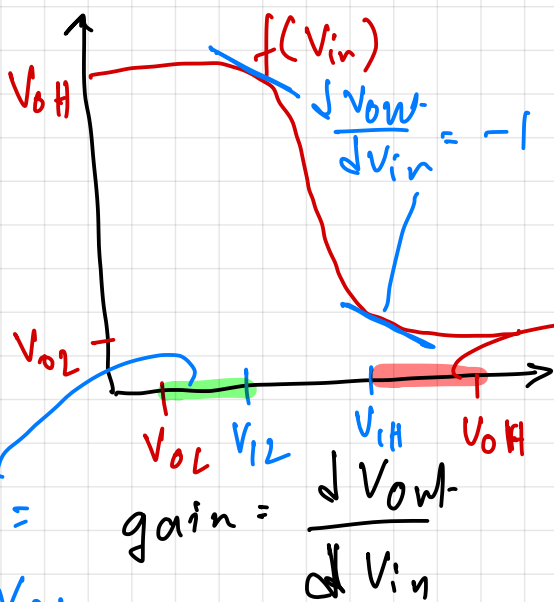



$$V_{OH} = f(V_{OL})$$

$$V_{OL} = f(V_{OH})$$

$$V_{OL} \neq 0$$

$$NM_H = V_{OH} - V_{IH}$$

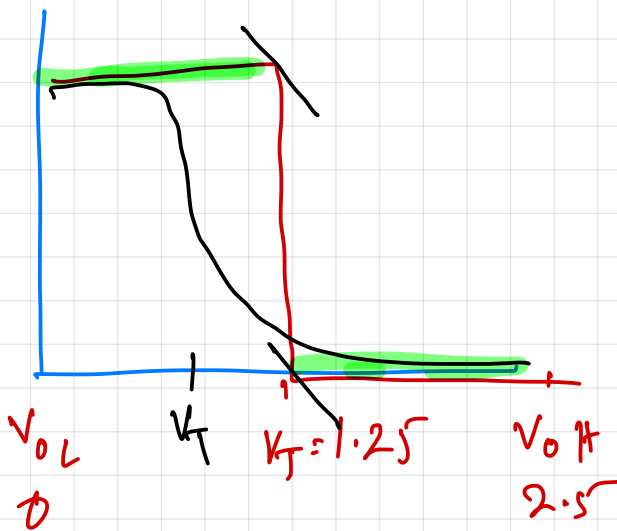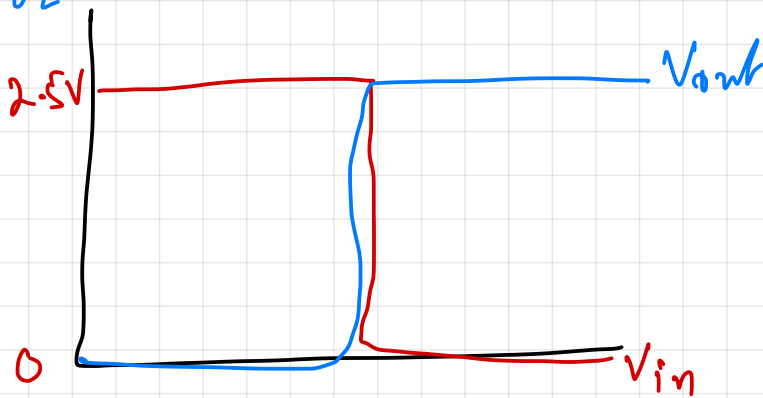
Any voltage above V_{IH} will be treated as high




$$NM_L = 1V$$

$$NM_H = 4V$$

$$V_M = V_{out} = V_{IN}$$

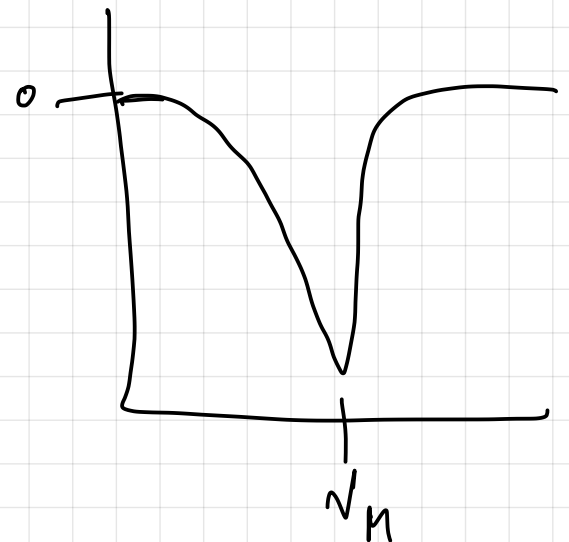


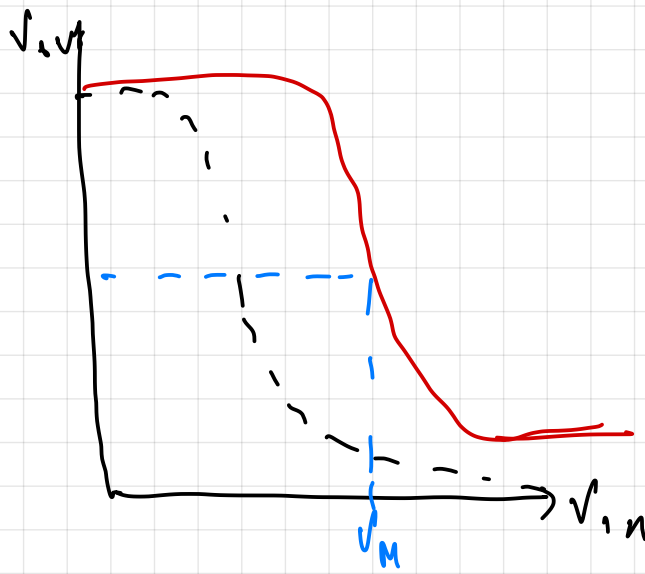

What happens when $R_L \uparrow$

$$V_{OL} = \frac{R_{ON}}{R_{ON} + R_L}$$

$R_L = 75 K\Omega$

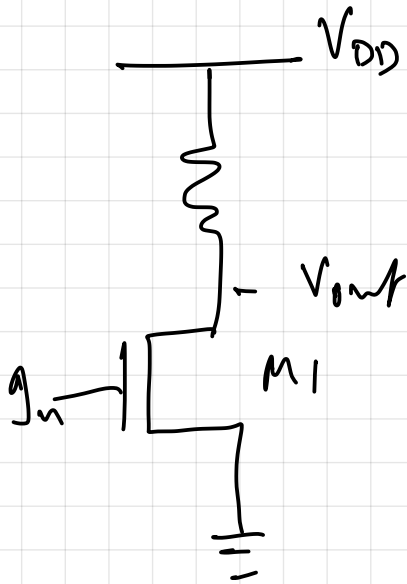

$W \uparrow \rightarrow I_D \uparrow$ Pull down is stronger
VTC shifts left

$R_L \uparrow$ pull up weaker relative to pull down \therefore VTC shifts left

