


# ANALOG LAB 2022

## EE2401


### Experiment 4: Charge pump

---

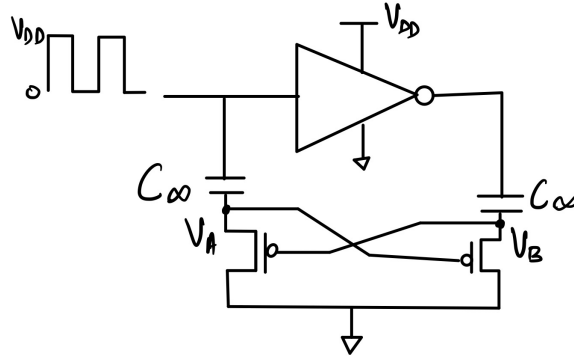1. Determine the voltage waveforms of  $V_A$  and  $V_B$  in steady state in the figure below. Analyze by hand taking into account region of operation for the transistors.



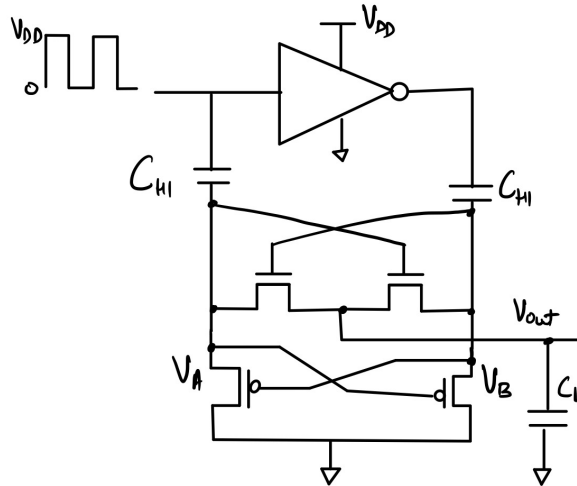2. NMOS transistors are added to multiplex  $V_A$  and  $V_B$  resulting in  $V_{out}$  as shown in figure below. Use CD4069 ICs to implement this circuit. Use the following values:
  - Clock frequency: 10 kHz
  - Supply voltage: 5 V
  - $C_{HI}$ : 10 nF



Simulate and find the output for  $C_L$  equal to 0 and 10 nF. Now replace  $C_L$  with a current load of 1 mA to ground. What do you observe?

3. Design and simulate a circuit that gives positive output of close to twice the supply voltage w.r.t. ground.

**CAD info:**

- Use model of the inverter provided in Experiment 1.
- CD4069 <https://www.ti.com/product/CD4069UB>
- PSPICE models can be used in LTspice using this procedure: <https://www.analog.com/en/technical-articles/ltspice-simple-steps-to-import-third-party-models.html>

**Submit the following:**

- Testbench snapshot, output plots
- Hand calculation
- Any unusual observation along-with comments